

EE2020

Digital Fundamentals

(L6: Logic IC families)

Prof. Massimo Alioto
Dept of Electrical and Computer Engineering
Email: *massimo.alioto@nus.edu.sg*

Outline

- Introduction to digital IC technologies
- Logic gate characteristics
- CMOS logic gates
- TTL logic gates
- Commercial logic families
- CMOS-TTL Interfacing

Logic gate characteristics

- **Static parameters**

- V_{OL} → Maximum Logic LOW output voltage
- V_{OH} → Minimum Logic HIGH output voltage
- V_{IL} → Maximum Logic LOW input voltage
- V_{IH} → Minimum Logic HIGH input voltage
- NM_H → Noise margin high
- NM_L → Noise margin low
- I_{OL}/I_{OH} → Logic LOW/HIGH output currents
- I_{IL}/I_{IH} → Logic LOW/HIGH input currents (for TTL only)
- Power dissipation


- **Dynamic parameters**

- Propagation delay
- Fan-out

EE2020 Digital Fundamentals - XU YP

3

V_{OH} , V_{OL} , V_{IH} , V_{IL}

 


- V_{OH} is minimum output voltage that establishes valid logic high to the following gate
- V_{OL} is the maximum output voltage that established valid logic low to the following gate
- V_{IH} is the minimum valid logic high input voltage
- V_{IL} is the maximum valid logic low input voltage

EE2020 Digital Fundamentals - XU YP

4

I_{OH} , I_{OL} , I_{IH} , I_{IL}

 


- I_{OH} is maximum current that can flow out of an output when output voltage maintains a valid logic high
- I_{OL} is the maximum current that can flow into an output when output voltage maintains a valid logic low
- I_{IH} is the current flowing into or out of an input when the input voltage is a valid logic high
- I_{IL} is the current flowing into or out of an input when the input voltage is a valid logic low

EE2020 Digital Fundamentals - XU YP

5

Noise margin (NM_H , NM_L)

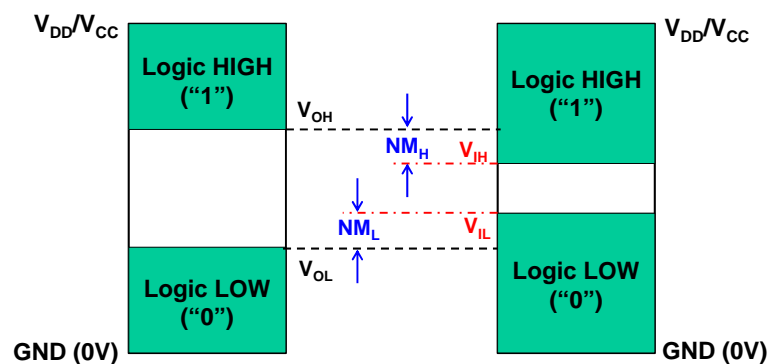

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$


EE2020 Digital Fundamentals - XU YP

6

Power Dissipation

- Represents the amount of power **needed by the gate**. Often expressed in mW (milliwatts).
- Calculated from the supply voltage V_{CC} and the current I_{CC} that is drawn by the circuit.
- Power dissipation $P_D = V_{CC} * I_{CC}$
- Current drawn depends on the logic state of gate.

Propagation delay

 

Fan-Out


- Determines how many standard loads can be connected to the output of a gate
 - A standard load is defined as the amount of current needed by an input of another gate in the same logic family
 - Loading is also used to indicate fan-out.
- The output of a gate can supply a limited amount of current. Above that it is said to be **overloaded**.
- Each input of a gate also requires current
- Each additional connection adds to the gate load
- Exceeding the maximum load may cause malfunction

EE2020 Digital Fundamentals - XU YP


9

Fan-Out

Output is logic HIGH:

 

Output is logic LOW:

 

- Calculated from the amount of current **available in the gate-output** to that is **needed in the input**.
- Fan-out = $\min(I_{OH}/I_{IH}, I_{OL}/I_{IL})$
- Example: standard TTL gates
 - $I_{OH} = 400 \mu A$, $I_{IH} = 40 \mu A$, $I_{OL} = 16 \text{ mA}$, $I_{IL} = 1.6 \text{ mA}$
 - Fan-out = $\min(400/40, 16/1.6) = 10$
 - The maximum number of gates that can be connected (or driven) is 10

EE2020 Digital Fundamentals - XU YP

10

Digital IC technologies



- Digital integrated circuits can be designed in different technologies
- Technology will impact on the performance of ICs
- The two mainstream technologies are
 - CMOS IC technology
 - Bipolar IC technology
- CMOS IC technology is based metal-oxide-semiconductor field-effect transistors (MOSFET)
- Bipolar IC technology is based on bipolar junction transistors (BJT)

EE2020 Digital Fundamentals - XU YP

11

MOSFET

n-MOSFET

  


$$I_D = I_S$$

$$I_D = f(V_{GS})$$

$$\Delta I_D = \frac{df(V_{GS})}{dV_{GS}} \Delta V_{GS}$$

Small V_{GS} change can induce large I_D change \rightarrow amplification

MOSFET is a voltage-controlled device

 


EE2020 Digital Fundamentals - XU YP

12

MOSFET

p-MOSFET

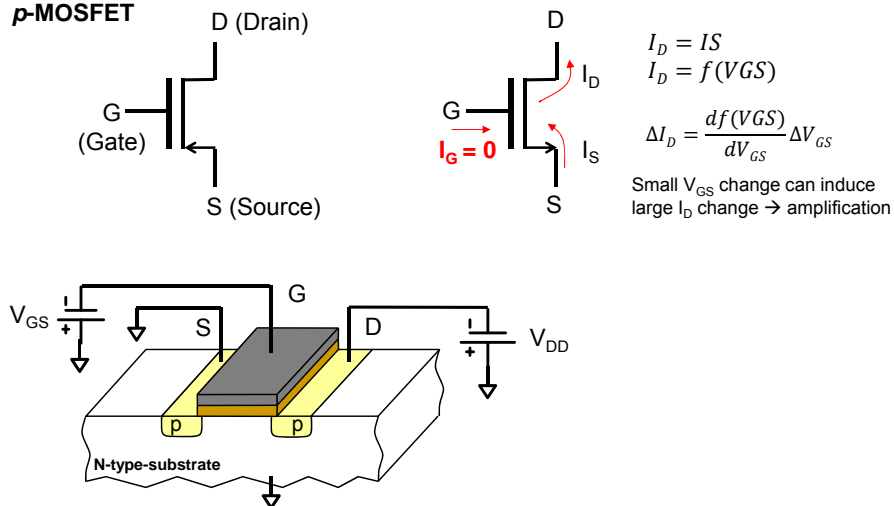

EE2020 Digital Fundamentals - XU YP

13

Logic ICs based on MOS technology

- **PMOS or NMOS**
 - The early MOS technology was based on either PMOS or NMOS only. It was later replaced by CMOS technology.
- **CMOS (Complementary MOS)**
 - Both NMOS and PMOS are used in the technology
 - CMOS static logic is used to implement logic gates
 - The advantages of CMOS static logic are
 - Full output swing from ground to supply voltage \rightarrow high noise margin;
 - There is always a low impedance path from the output to ground or supply voltage
 - No static power dissipation (only one transistor is on)
 - No static input current \rightarrow very high input impedance (input is capacitive)


EE2020 Digital Fundamentals - XU YP

14

Transistor as a switch


- In this part, we consider an MOS transistor (MOSFET) as a switch
- MOS transistors can be either NMOS or PMOS transistors
- We view a 3-terminal MOSFET as a blackbox whose drain and source terminals are equivalent to the two terminals of an ordinary switch and the gate controls the switch

NMOS transistor:

 


$V_G = V_{DD}$ ("1") → NMOS is **on** (switch closed)
 $V_G = 0V$ ("0") → NMOS is **off** (switch open)

PMOS transistor:

 

$V_G = 0V$ ("0") → PMOS is **on** (switch closed)
 $V_G = V_{DD}$ ("1") → PMOS is **off** (switch open)

CMOS logic gates

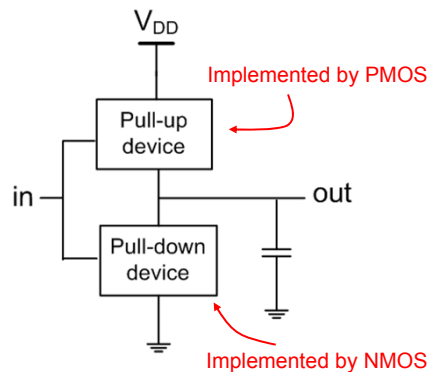


Recall → Features of CMOS static logic:

- Full output swing from ground to supply voltage → high noise margin;
- There is always a low impedance path from the output to ground or supply voltage
- No static power dissipation (only one transistor is on)
- No static input current → very high input impedance (input is capacitive)

CMOS NOT Gate (Inverter) and Buffer

 $V_G = V_{DD}$ ("1") → PMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch
 $V_G = 0V$ ("0") → PMOS turns **ON** (D and S short circuit) → equivalent to a **closed** switch



Physical truth table:


V_G	V_o
0V	V_{DD}
V_{DD}	0V




Logic truth table:

V_G	V_o
0	1
1	0

Inverter:

 

Buffer:

 


$V_G = V_{DD}$ ("1") → NMOS turns **ON** (D and S short) → equivalent to a **closed** switch
 $V_G = 0V$ ("0") → NMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch

EE2020 Digital Fundamentals - XU YP

17

CMOS NAND gate

 $V_G = V_{DD}$ ("1") → PMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch
 $V_G = 0V$ ("0") → PMOS turns **ON** (D and S short circuit) → equivalent to a **closed** switch




Physical truth Table:

V_{G1}	V_{G2}	V_o
0V	0V	V_{DD}
V_{DD}	0V	V_{DD}
0V	V_{DD}	V_{DD}
V_{DD}	V_{DD}	0



Logic truth Table:

V_{G1}	V_{G2}	V_o
0	0	1
1	0	1
0	1	1
1	1	0

 


$V_G = V_{DD}$ ("1") → NMOS turns **ON** (D and S short) → equivalent to a **closed** switch
 $V_G = 0V$ ("0") → NMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch

EE2020 Digital Fundamentals - XU YP

18

CMOS NOR gate

 $V_G = V_{DD}$ ("1") → PMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch
 $V_G = 0V$ ("0") → PMOS turns **ON** (D and S short circuit) → equivalent to a **closed** switch



Physical truth Table:

V_{G1}	V_{G2}	V_o
0V	0V	V_{DD}
V_{DD}	0V	0
0V	V_{DD}	0
V_{DD}	V_{DD}	0

Logic truth Table:



V_{G1}	V_{G2}	V_o
0	0	1
1	0	0
0	1	0
1	1	0

NOR gate: V_1 V_2 $V_o = \overline{V_1 + V_2}$


$V_G = V_{DD}$ ("1") → NMOS turns **ON** (D and S short) → equivalent to a **closed** switch
 $V_G = 0V$ ("0") → NMOS turns **OFF** (D and S open circuit) → equivalent to an **open** switch

Bipolar Junction transistor (BJT)

NPN BJT

  




BJT is a current-controlled device

 

Cross section of BJT IC technology

Bipolar Junction transistor – cont.

PNP BJT

   

Cross section of BJT IC technology

EE2020 Digital Fundamentals - XU YP

21

Logic ICs based on BJT IC technology

- **TTL** (Transistor-Transistor Logic)
 - Invented by TRW Inc. in US, first commercial TTL logic IC was introduced by Sylvania in 1963 and became popular with Texas Instrument's 5400 and 7400 series
- **ECL** (Emitter-Coupled Logic)
 - Invented by IBM, first commercial integrated-circuit ECL family was introduced by Motorola in 1962
 - Suitable for high-speed logic circuits

EE2020 Digital Fundamentals - XU YP

22

TTL logic gates

Features of TTL logic gates

- Based on BJTs
- Most widely used logic ICs at gate or MSI level
- Typically operated under 5V supply voltage
- Having different series that optimized for low power, high speed, etc
- Inputs of the gate draw static current
- Due to lack of prerequisite, we'll not discuss circuit details of TTL logic gates

Commercial logic families

- 74xxx Series
 - TTL family (Transistor-Transistor Logic)
 - Use Bipolar or CMOS technology
- Name convention
 - 1st field: 2 or 3 letters → Manufacturer (sometimes omitted)
 - 2nd field: 74 → Commercial temperature range (54 → Military)
 - 3rd field: 4 letters → Logic sub-family
 - 4th field: 2 or more digits → Type of device
 - 5th field: Type of package or other information (sometimes omitted)

DM 74 LS 14 N

↓
National Semiconductor

↓
Commercial temperature range

↓
Low power shottky

↓
Hex inverters with schmitt trigger inputs

↓
Plastic package

74 series Logic Sub-families (3rd field)


- TTL (Bipolar)
 - 74L → Low power
 - 74H → High speed
 - 74LS → Low power Schottky
 - 74AS → Advanced low power schottky
 - 74ALS → Advanced low power schottky
 -
- CMOS (not TTL, but retains some compatibility)
(same part numbers as bipolar are retained to identify the function)
 - 74C → CMOS 4-15V
 - 74HC → High speed
 - 74AC → Advanced CMOS
 - 74LVC → Low voltage, 1.65 to 3.3V
 - 74LVX → 3.3V with 5V tolerant inputs
 -

EE2020 Digital Fundamentals - XU YP


25

Some 74 series Logic gates


7400 (74HC00)
(Quad 2-input NAND gate)

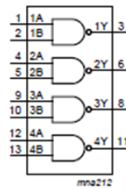


7410(74HC10)
(Dual 3-input AND gate)

 


7421(74HC21)
(Dual 4-input AND gate)

 


7402(74HC02)
(Quad 2-input NOR gate)

 

7427(74HC27)
(Quad 3-input NOR gate)

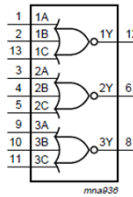

7404(74HC04)
(Hex inverters)

 

EE2020 Digital Fundamentals - XU YP

26

CMOS logic family

- **4000(RCA)/14000 (Motorola)**
 - Very low power dissipation.
 - Operate over wide power supply range (3 to 15V).
 - **Slow** compared to TTL and other CMOS series.
 - Very low output current capability.
 - **Not pin compatible with TTL**
 - This very first series of CMOS is **rarely used** now.
- **74C**
 - **Pin compatible & functionally equivalent to TTL** devices with same number.
 - Many TTL functions are available in this series.
 - Same performance as 4000 series.

EE2020 Digital Fundamentals - XU YP

27

CMOS logic family (cont.)

- **74HC/HCT (High speed CMOS)**
 - Improved version of 74C series. Its speed about same as TTL 74LS series, much higher current capability than 74C series.
 - 74HCT devices are voltage compatible with TTL but 74HC devices are not.
- **74AC/ACT (Advanced CMOS)**
 - **Functionally equivalent to various TTL** series, but **not pin compatible**.
 - Pin incompatibility because pin placements chosen for **better noise immunity**.
 - ACT series offers better noise immunity, less propagation delay, and higher maximum clock speed.
- **74AHC (Advanced high-speed CMOS)**
 - Newest CMOS series, replacement for HC devices.
 - For **faster, lower power** applications.

EE2020 Digital Fundamentals - XU YP

28

CMOS/TTL Comparison (static)

Input/output voltage levels (in volts) with $V_{DD} = V_{CC} = +5\text{ V}$.

Parameter	CMOS							TTL			
	4000B	74HC	74HCT	74AC	74ACT	74AHC	74AHCT	74	74LS	74AS	74ALS
V_{IH} (<i>min</i>)	3.5	3.5	2.0	3.5	2.0	3.85	2.0	2.0	2.0	2.0	2.0
V_{IL} (<i>max</i>)	1.5	1.0	0.8	1.5	0.8	1.65	0.8	0.8	0.8	0.8	0.8
V_{OH} (<i>min</i>)	4.95	4.9	4.9	4.9	4.9	4.4	3.15	2.4	2.7	2.7	2.7
V_{OL} (<i>max</i>)	0.05	0.1	0.1	0.1	0.1	0.44	0.1	0.4	0.5	0.5	0.4
V_{NH}	1.45	1.4	2.9	1.4	2.9	0.55	1.15	0.4	0.7	0.7	0.7
V_{NL}	1.45	0.9	0.7	1.4	0.7	1.21	0.7	0.4	0.3	0.3	0.4

Noise margin H and L

EE2020 Digital Fundamentals - XU YP

29

CMOS/TTL Comparison (Dynamic)

Parameter	4000B	74HC/HCT	74AC/ACT	74AHC/T	74	74LS	74AS	74ALS	ECL
Power dissipation Per gate (mW)									
Static	1.0×10^{-3}	2.5×10^{-3}	5.0×10^{-3}	9.0×10^{-3}	10	2	8	1.2	25
at 100 kHz	0.1	0.17	0.08	0.006	10	2	8	1.2	25
Propagation delay (ns)	50	8	4.7	3.7	9	9.5	1.7	4	1
Speed-power (at 100 kHz) (pJ)	5	1.4	0.37	0.02	90	19	13.6	4.8	25
Maximum clock rate (MHz)	12	40	100	130	35	45	200	70	300
Worst-case noise margin (V)	1.5	0.9	0.7	0.55	0.4	0.3	0.3	0.4	0.25

30

Summary

- Digital IC technology
 - BJT and MOSFET
 - BJT and CMOS technology
- CMOS logic gates
 - Implementation of NOT, NAND, NOR, AND and OR gates
- Commercial logic families
 - TTL and CMOS
- Logic gate characteristics
 - Static parameters (V_{OH} , V_{OL} , V_{IH} , V_{IL} , I_{OH} , I_{OL} , I_{IH} , I_{IL} , NM_H , NM_L and P_D)
 - Dynamic parameters (t_p and fan-out)
 - CMOS/TTL comparison
- Logic family interfacing (TTL driving CMOS, CMOS driving TTL)