

## Tutorial Questions (Part 2 continued)

**ASM** State Machine Design


Please attempt the *self-study questions* (labeled “SS”).

20. A state machine’s output **Q** depends on the value of an input signal **X** in the *current* and *previous clock cycles*, i.e.,  $X_t$  and  $X_{t-1}$  as specified below:

$X_t$	$X_{t-1}$	$Q^+$
0	0	$\bar{Q}$
0	1	1
1	0	0
1	1	Q

Design the state machine using (a) J-K flip-flops and (b) D flip-flops. Does one design need more components than the other? Why?

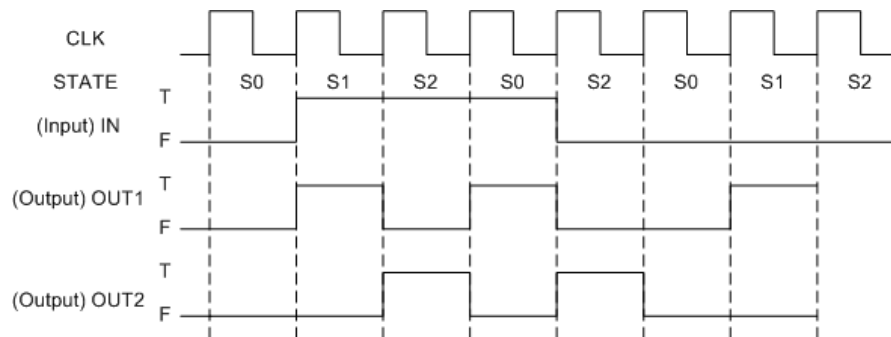21. For the state machine with the timing diagram shown in the figure below:
- draw its functional block diagram clearly showing the input & output signals,
  - construct the *ASM* chart,
  - determine the next state table,
  - draw a detailed circuit diagram showing the realization of the state machine in the traditional method using D flip-flops, and
  - write a *VHDL* description (i.e., program) for the state machine.



**SS10.** A **3-bit synchronous counter** counts in one of two sequences depending on a 1-bit *synchronous control input*, **EVEN**. When **EVEN** is false, the counter behaves as a *normal 3-bit mod-8 up-counter*, otherwise it counts in the sequence: .. 0, 2, 4, 6, 0, 2 ...

- What is meant by “*synchronous input*”?
- Draw the *ASM* chart for the counter.
- If the counter’s current output is “2”, under what conditions will it output “3” in the next state?
- Implement the counter using *D-Flip-flops* and any additional logic devices. Clearly show the steps in your design and verify the correct operation of the counter.

- (e) Using additional logic circuits, show how you would incorporate a “terminal count” output, TC, which is asserted if the state is 7 and EVEN=0, or if the state is 6 and EVEN=1.

22. Given the *ASM* chart of a state machine shown in Figure (a) below,
- complete the corresponding timing diagram in Figure (b),
  - construct the next state table for the state machine,
  - draw a detailed circuit diagram showing the realization/implementation of the state machine in the **traditional method**,
  - draw a detailed circuit diagram showing the realization/implementation of the state machine in the **PLA method** using a PLA device with 4 inputs, 4 outputs and 8 product terms.

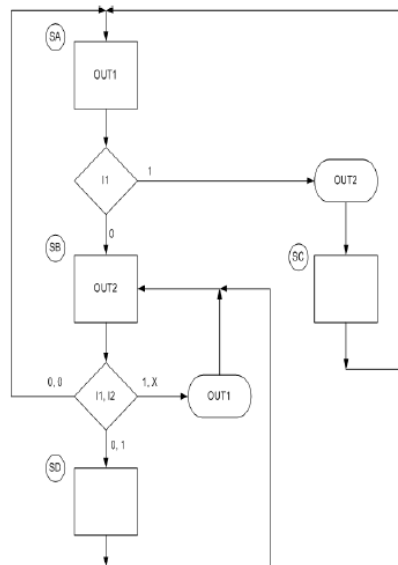


Figure (a)


 


Figure (b)

23. Given the *ASM* chart below:

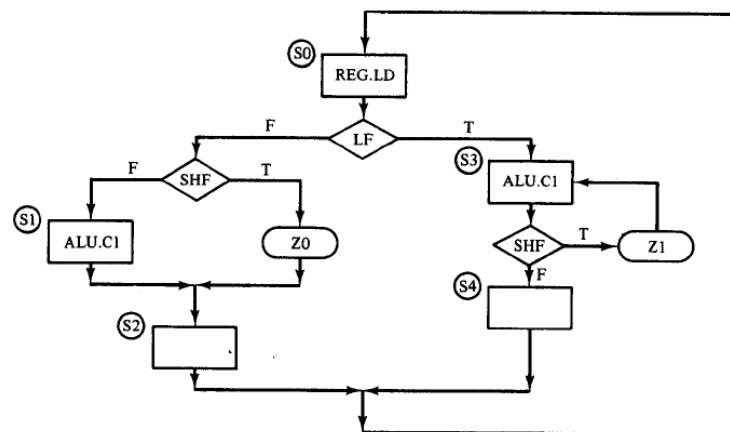

- (a) Draw a functional block diagram of the state machine.
  - (b) Draw a block diagram of the state generator, clearly showing the inputs, outputs, and the state flip-flops (D-FFs).
  - (c) Noting that ROMs can be used to realize *combinational logic functions*, realize the state machine by using a ROM. Draw the entire circuit, clearly showing all ROM connections and the ROM contents in hexadecimal form.
24. A digital circuit is to be designed to implement the “snooze” function of an alarm clock. The circuit signals are as follows:
- Synchronous Inputs:** RING, RESET.
- Output:** ALARM

The circuit remains in the “wait” mode until input RING is asserted for one clock period, at which time the circuit goes into the “snooze” mode by asserting ALARM for 10 seconds, waiting for 5 minutes and continuously repeating this cycle until the user resets the circuit causing RESET to be asserted for one clock period.

Derive the *ASM* chart and identify the *architectural elements* (i.e., list the elements and their functions) required for a hardware realization of this state machine. Write a *VHDL* program which realizes this state machine. You may assume that an accurate 1Hz clock is available as input.

**SS11.** A digital circuit has to be designed to find the number of 1’s in an 8-bit input data.

The operation of this circuit is specified as follows: When the input START becomes 1 (for one clock cycle), an 8-bit number is input into the circuit one-bit per consecutive clock cycle via the circuit’s 1-bit input DATA. The circuit evaluates and outputs X, a 3-bit output signal which is the number of 1’s received up to the current instant. After the 8-bits have been received, the circuit asserts the output signal DONE and clears X.

Derive the *ASM* chart for this circuit. Write a *VHDL* program which realizes the circuit and verify its performance using available simulation tools.

25. A synchronous state machine needs to be designed to *count people entering and leaving a room*. The room has a *separate* entrance and exit. Each is equipped with a sensor to detect people *coming in through the entrance* or *leaving through the exit*. The sensors provide signals ENTER (when a person enters) and LEAVE (when a person exits), which are **TRUE** for one clock period. The entrance and exit are each narrow enough for only one person to pass through at a time, but it is possible for one person to enter *while* another is exiting during one clock period. The machine should output an EMPTY signal when nobody is in the room and a FULL signal when there are 3 people (*the maximum allowed*) in the room. The EMPTY and FULL signals should be asserted as soon as the conditions are satisfied, i.e. before the next active clock transition. Nobody will be allowed into the room while FULL is asserted. Derive the *ASM* chart and write a *VHDL* program which realizes this state machine. You may assume that an accurate 1Hz clock is available as input.