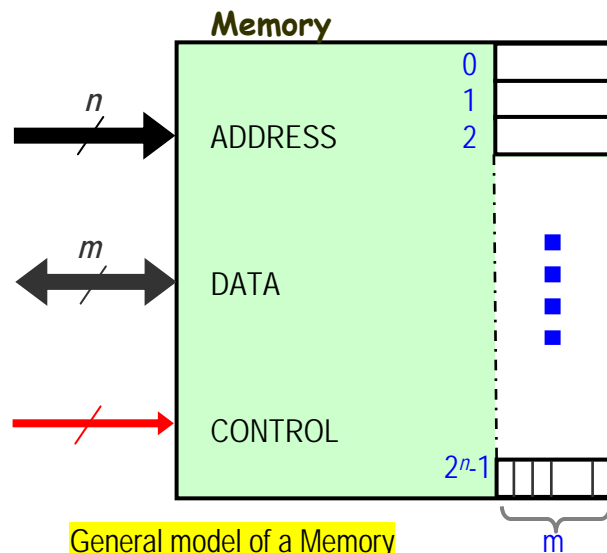



Memory **Devices**

© Copyright *Ashraf Kassim*. All rights reserved.

Memories ...



General model of a Memory

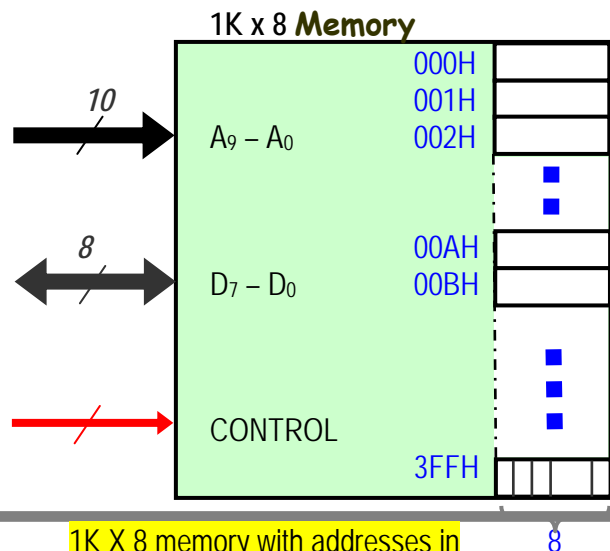


1K X 8 memory with addresses in Hexadecimal

- A memory unit has a number of **locations** where **data** can be stored.
- Generally, **data** can be read from or written into memory locations. The operation to be performed is specified by the **control** signal.
- Each memory location has a **unique address** associated with it which is specified by the signals coming in on the **address lines**.
- If **n** address lines are available, then **2ⁿ memory locations**, 0, 1, ..., 2ⁿ-1 can be accessed directly.
- These memories have **random access** capability.
- If the unit has **m** data lines, then each location can store **m** bits of **data**.
- The **capacity** of a memory unit is the product of the **number of memory locations** & the number of bits per location, **2ⁿ x m**.
- **Data lines** can be bidirectional to permit **read/write** into memory locations. Such memories are called Read-Write Memories. (**RWM**)

$1K = 2^{10} = 1024$ {0th to 1023th memory locations : 000H to 3FFH }
 $2K = 2^{11} = 2048$ {0th to 2047th memory locations : 000H to 7FFH }
 $4K = 2^{12} = 4096$ {0th to 4095th memory locations : 000H to FFFH }

 Memories ... *RAMs* (random access memory)



- **Address lines & control lines** are always unidirectional \Leftrightarrow
- If data lines are also unidirectional \Rightarrow , then data can only be read from memory. Such devices are called **read only memories** (*ROMs*).
- **Access time** is a measure of the memory's operating speed.
- Memories that are commonly called *RAMs* (*random access memories*) are really **read/write** memories (*RWMs*).


Static RAMs (*SRAMS*)

- basically Flip-Flops made with bipolar semiconductor technology
- tend to be **very fast**, but consume a lot of power. Hence are mainly used as cache memory in computers.
- Static memories store data until powered off.
- Bipolar devices are comparatively large, & hence packing density is not very high.


Dynamic RAMs (*DRAMs*)

- are basically capacitors that store charge and are made with MOS semiconductor technology.
- tend to lose charge (data) due to leakage even when powered on. Hence they have special circuitry to refresh the capacitors with charge. Hence the name dynamic.
- Packing density is very high and hence very large capacities can be obtained on a single chip.

 
Both *SRAMS* and *DRAMs* are **volatile** memories, i.e., they lose their contents when powered off.





RAM configuration... 16 x 8 example...

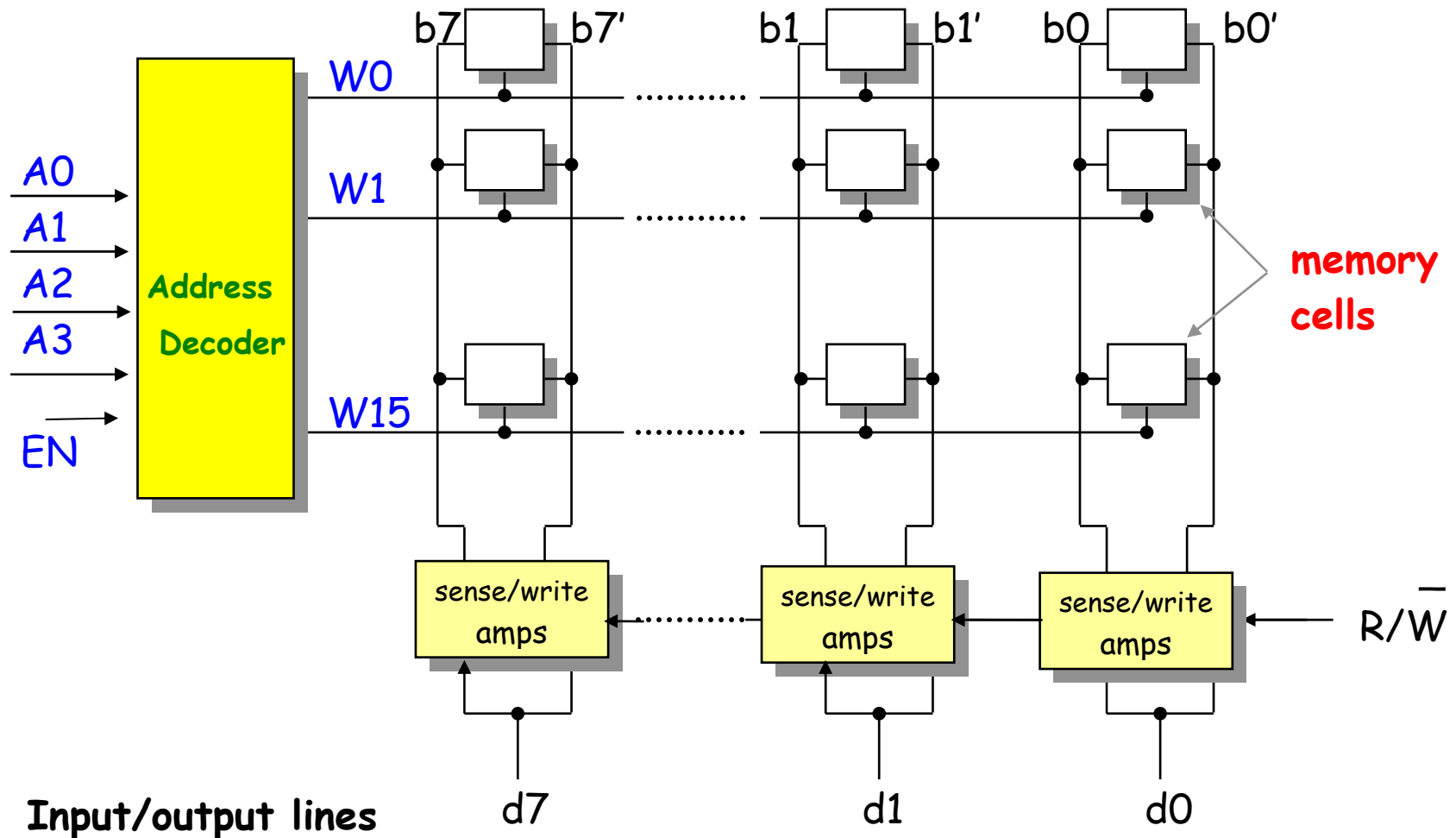

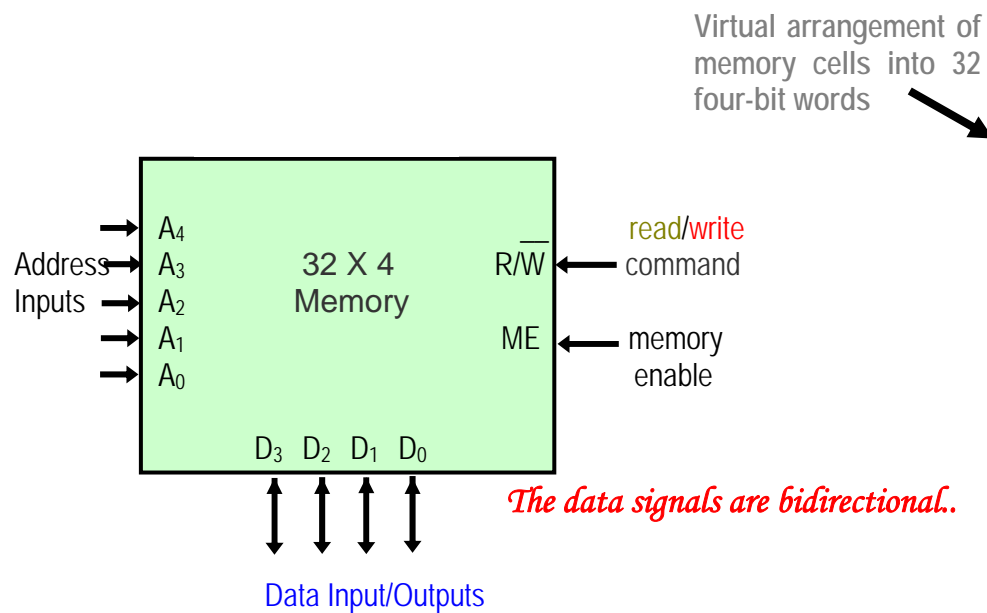
Example: A 32 x 4 *RWM* (*SRAM* or *DRAM*)



	ADDRESS		Memory Cells			
	hex	binary				
0	00H	0 0 0 0 0	1	1	0	1
1	01H	0 0 0 0 1	0	1	0	1
2	02H	0 0 0 1 0	1	0	0	1
3	03H	0 0 0 1 1	1	1	1	0
4	04H	0 0 1 0 0	0	0	1	1
...						
28	1CH	1 1 1 0 0	0	1	0	0
29	1DH	1 1 1 0 1	1	0	0	1
30	1EH	1 1 1 1 0	1	1	0	1
(2 ⁵ -1) 31	1FH	1 1 1 1 1	0	1	1	0

  

Memories ... *ROMs* (read only memory)

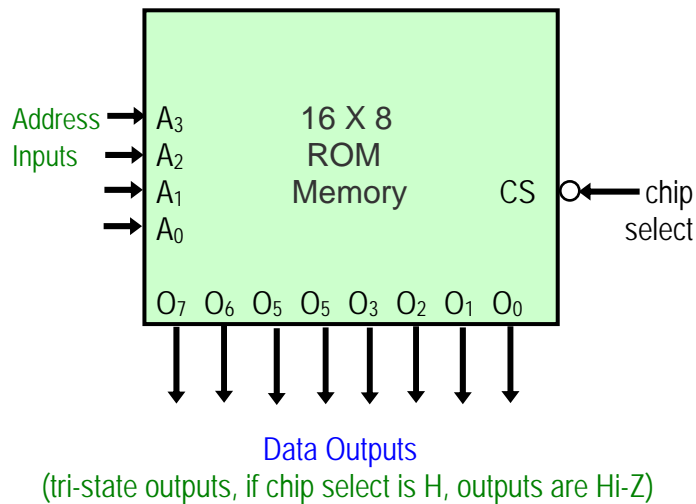

- During normal operation data can be read from *ROMs* memory location, but **cannot** be written into.
- Principal advantage of *ROM* over *RAM* is that stored data will be retained after power off.
- Types of *ROMs*
- Different types of *ROMs* are available.
 - Normal read operations for all types is same.
 - Programming/Erasing/Re-programming is different

Mask Programmed *ROM*

- **Programmed by manufacturer** according to customer specs.
- A photographic negative called a mask is used to control electrical connections.
- Once programmed, no changes possible.
- A custom mask is produced for each design, hence economical only if manufactured in large volumes.

Field Programmable ROM *PROM*

- **User programmable.** Has fusible links (like PLA & PALs) which can be broken (intact fuse = 1, blown fuse = 0).
- Can be programmed only once. Done by commercially available programming devices.
- Suitable for low volume applications.

Erasable Programmable ROM *EPROM*

- Can be **erased & re-programmed** as many times as desired.
- Erasing takes place by exposing *EPROM* to UV light. 15-30 min to erase all data.
- can be programmed by commercial programmers.
- Ideal for prototype implementation

Electrically Erasable PROM *EEPROM*

- Unlike *EPROMs*: **individual** words can be electrically erased & re-programmed.
- Entire *EEPROM* can be **erased in ~10ms**
- Since erasing/re-programming is done electrically, need not remove chip from circuit to do so.
- Relatively fast (access time ~ 250 ns)


ROMs are **non-volatile** memories, i.e., they don't lose their contents when powered off.

ROM example...

A 16 x 8 ROM:

Word	Address				Data							
	A3	A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	1	1	0	1	1	1	1	0
1	0	0	0	1	0	0	1	1	1	0	1	0
2	0	0	1	0	1	0	0	0	0	1	0	1
3	0	0	1	1	1	0	1	0	1	1	1	1
4	0	1	0	0	0	0	0	1	1	0	0	1
5	0	1	0	1	0	1	1	1	1	0	1	1
6	0	1	1	0	0	0	0	0	0	0	0	0
7	0	1	1	1	1	1	1	0	1	1	0	1
8	1	0	0	0	0	0	1	1	1	1	0	0
9	1	0	0	1	1	1	1	1	1	1	1	1
10	1	0	1	0	1	0	1	1	1	0	0	0
11	1	0	1	1	1	1	0	0	0	1	1	1
12	1	1	0	0	0	0	1	0	0	1	1	1
13	1	1	0	1	0	1	1	0	1	0	1	0
14	1	1	1	0	1	1	0	1	0	0	1	0
15	1	1	1	1	0	1	0	1	1	0	1	1

Word	Address				Data							
	A3	A2	A1	A0	D7-D0							
0				0	DE							
1				1	3A							
2				2	85							
3				3	AF							
4				4	19							
5				5	7B							
6				6	00							
7				7	ED							
8				8	3C							
9				9	FF							
10				A	B8							
11				B	C7							
12				C	27							
13				D	6A							
14				E	D2							
15				F	5B							

 

Data Outputs (tri-state)
(if chip select is 0, outputs are Hi-Z)

ROM applications...

Microcomputer program storage (firmware): ROM stores control program needed for computer operation e.g. electronic games, cash registers, etc.


Bootstrap memory (BIOS): Most computers store their OS on hard disk, not ROM. On power-up, CPU accesses ROM which has a small **bootstrap** program which: initializes system hardware, loads OS into RAM from hard disk, etc.

Data conversion: Convert data from one type of code to another, e.g. conversion of BCD code to drive 7-segment displays.

Alternatively, this example can be viewed as a systematic realization of a complex combinational circuit.

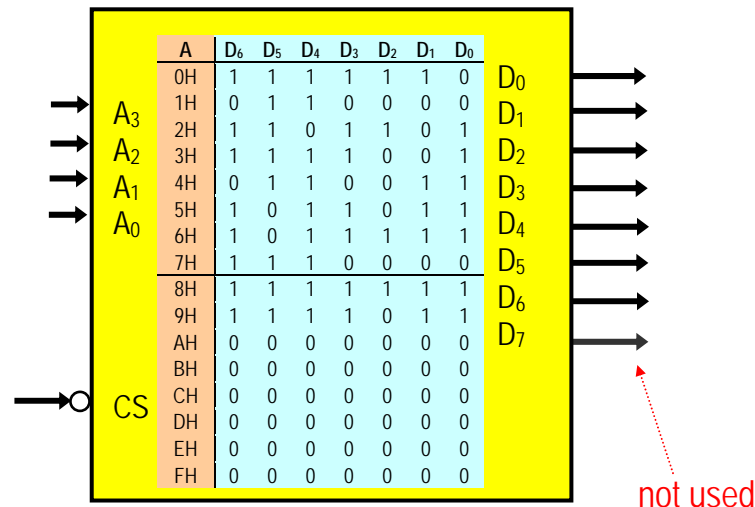Example illustrates that ROMs can also be used for realizing logic functions.

PROMs are closely related to PLA/PALs have hardwired AND and programmable OR gates.



Expanding word size and capacity...



Usually several memory devices/chips have to be combined for a desired **word size** and/or **capacity**.

Example: Design the following memory modules using only **1Kx4 RAM memory devices** for use in **12-bit memory address system**: →

- A block of 1K x 8 RAM memory from address 800H
- A block of 2K x 4 RAM memory from address 800H

Truth table of 1K x 4 RAM:

Operation	CS	WE
Hi-Z outputs	H	X
Read	L	H
Write	L	L

 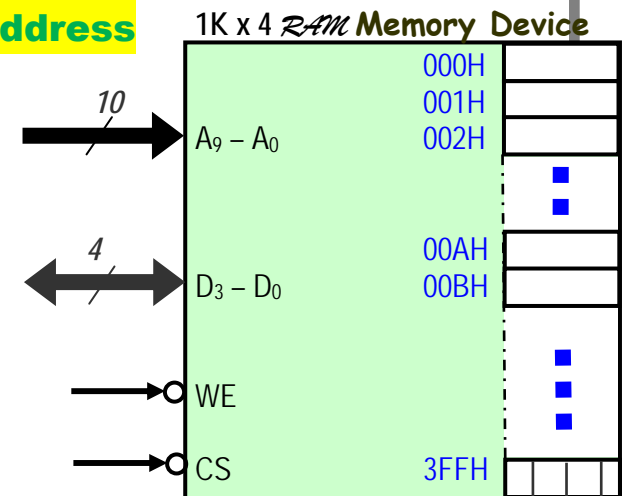

12-bit address memory system:
A₁₁ to A₀ : 000H to FFFH →

Expanding word size ...1Kx8 from two 1Kx4 Devices

1Kx8 from two 1Kx4 Devices: 800H to BFFH (12-bit address lines)

Memory Addresses:



1000 0000 0000
1000 0000 0001

...

1001 1000 0000

...

1011 1111 1111

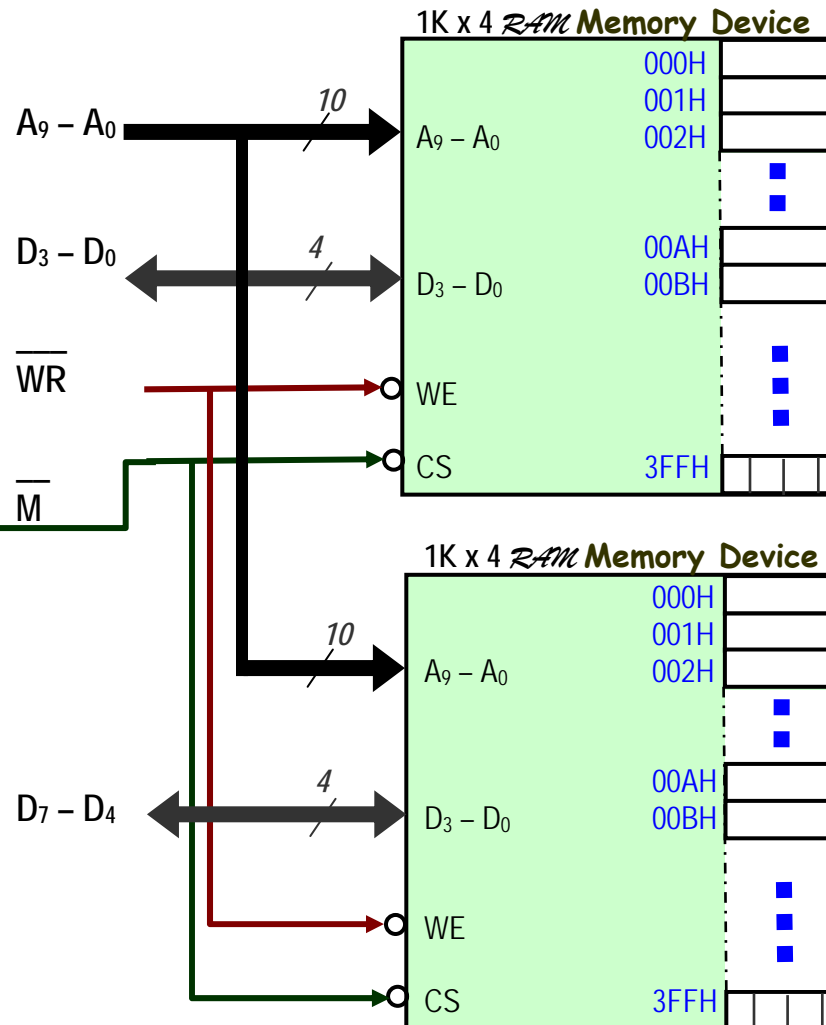 

Expanding capacity... 2Kx4 from two 1Kx4 Devices


2Kx4 from two 1Kx4 Devices: 800H to FFFH (12-bit address lines)

Memory Addrs: (800H to BFFH)

1000 0000 0000

⋮

1011 1111 1111

 


Memory Addrs: (C00H to FFFH)


1100 0000 0000

⋮


1111 1111 1111

 

1K x 4 RAM Memory Device

 


1K x 4 RAM Memory Device

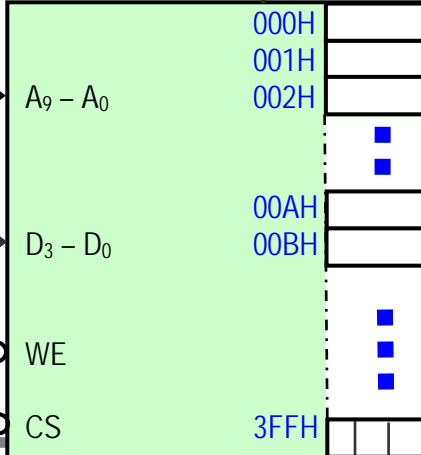

Exhaustive Decoding... decode all address lines...

 A 20-bit address system has a 8K ROM from 00000H & 4K RAM from 02000H.




memory map

Step#1: Write memory map (complete address range) of each memory module in hex/binary form:

A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	(HEX)
0000	0000	0000	0000	0000	ROM	00000H
0000	0001	1111	1111	1111		01FFFH
A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	(HEX)
0000	0010	0000	0000	0000	RAM	02000H
0000	0010	1111	1111	1111		02FFFH


Step#2: Decode address bits to select/enable memory modules. All address bits of the memory system have to be decoded.

RAM/ROM Decoding:

 

Exhaustive Decoding... decode ALL address lines...

 A 20-bit address system has a 8K ROM from 00000H & 4K RAM from 02000H.




Step#1: Write memory map (complete address range) of each memory module in hex/binary form:

A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	(HEX)
0000	0000	0000	0000	0000	ROM	00000H
0000	0001	1111	1111	1111		01FFFH
A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	(HEX)
0000	0010	0000	0000	0000	RAM	02000H
0000	0010	1111	1111	1111		02FFFH

Step#2: Decode address bits to select/enable memory modules. All address bits of the memory system have to be decoded.

What happens if not all addresses are decoded????

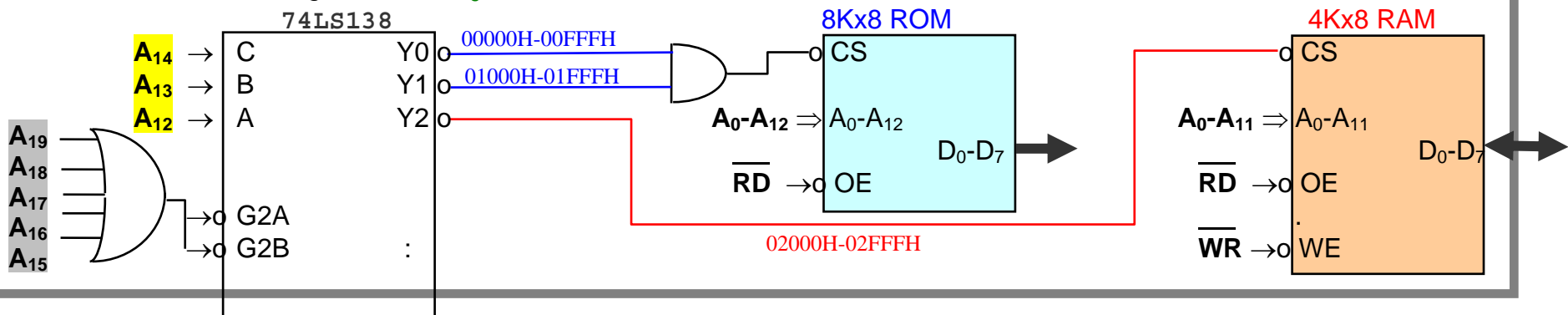RAM/ROM Decoding: (Solution using decoders)




In-exhaustive Decoding... **not all** address lines are decoded

A **20-bit address system** has a **8K ROM** from **00000H** & **4K RAM** from **02000H**.

memory map

 Step#1: Write memory map (complete address range) of each memory module in hex/binary form:



A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	(HEX)
XXXX	0000	0000	0000	0000	ROM	X0000H
XXXX	0001	1111	1111	1111		X1FFFH
A19-A16	A15-A12	A11-A08	A07-A04	A03-A00	DEVICE	
XXXX	0010	0000	0000	0000	RAM	X2000H
XXXX	0010	1111	1111	1111		X2FFFH

Step#2: Decode address bits to select/enable memory modules. *All* address bits of the memory system have to be decoded.

Each memory location has 16 addresses...

RAM/ROM Decoding: (Solution using decoders)

