
 


# *Programmable Logic Devices*


© Copyright *Ashraf Kassim*. All rights reserved.
 
## Motivation for *Programmable Logic Devices*

- Complex digital circuits require many such combinational circuits requiring many such SSI/MSI components
- Modern circuits rarely use SSI devices to implement logic systems.




# Programmable Logic Arrays

 

- Combinational circuits are realized as two-level **sum of products** (**SOP**), **AND-OR-INVERT** structures such as

$$Z = A\bar{B}CD + AB\bar{C}D + \dots$$

 - Programmable array block diagram for **SOP** form:



- PLDs incorporate many **AND-OR-INVERT** and other structures with programmable interconnections.

# Programmable Logic Arrays (*PLAs*)


Programmable Logic Array (PLA):

AND & OR arrays are programmable  $\Rightarrow$

AND plane produces **product terms**, OR plane realize **sum of product terms**.

Commercial *PLAs*:

 
- come in different sizes, with many more AND and OR terms.
- Either mask programmed by manufacturer or user programmed (**Field Programmable** *PLAs* – **FPLAs**).



**Note:**  $n$  inputs implies  $2^n$  possible product terms:  
 $A'B'C'$ ,  $A'B'C$ ,  $A'BC'$ ,  $A'BC$ ,  
 $AB'C'$ ,  $AB'C$ ,  $ABC'$ ,  $ABC$
 
## PLDs: Programming & Short hand notation ...

A PLD comes with all fuses (~) intact and the fuses are selectively “**blown**” during programming. The intact fuses are shown by **x**’s.



OTP



PLD is inserted into a *programming device* which is connected to a PC. User specifies logic functions to be **realized** on (e.g. VHDL based) software running on PC. The software generates a fuse map which specifies the **fuses** that are to be **blown** & those to be left **intact** to realize specified logic functions.

**Fuse map** is downloaded to *programming device*, which then blows the specified **fuses** and tests the programmed PLD for correct operation → *done!*
  
# Programmable Logic Arrays (PLAs)


AND inputs are “pulled-up” high while OR inputs are “tied” low through resistors.

PLDs: AND, OR inputs gate inputs are depicted as **single lines**:




 
# Programmable Read Only Memory (*PROM*)

A programmable read only memory or *PROM* has a fully decoded **AND** array (all **AND** terms decoded) & a completely flexible **OR** array (unlike *PAL*).




 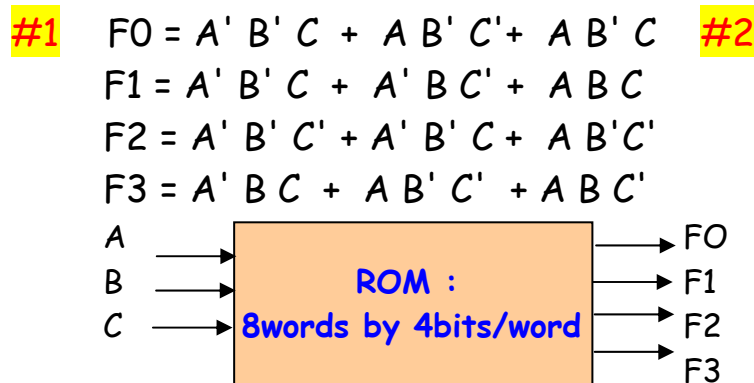Combinational logic implementation using a *PROM*:


 
## PLDs: PROM, PLA & PAL

PLDs incorporate many **AND-OR-INVERT** and other structures with programmable interconnections. **Programming the interconnections** in a PLD results in different logic implementations.





# Commercial PLDs


A PAL16R8 PLD  $\Rightarrow$

- 8 pdt terms to D input of FFs
- common clock (+ve edge) and tri-state enable for all
- Q output is feedback to AND array
- applications: counters SMs, etc

Conventional PLDs require a programmer & are either OTP (*one-time programmable*) or **UV Erasable**:

Electrically Erasable PLDs: can be programmed & erased in place:

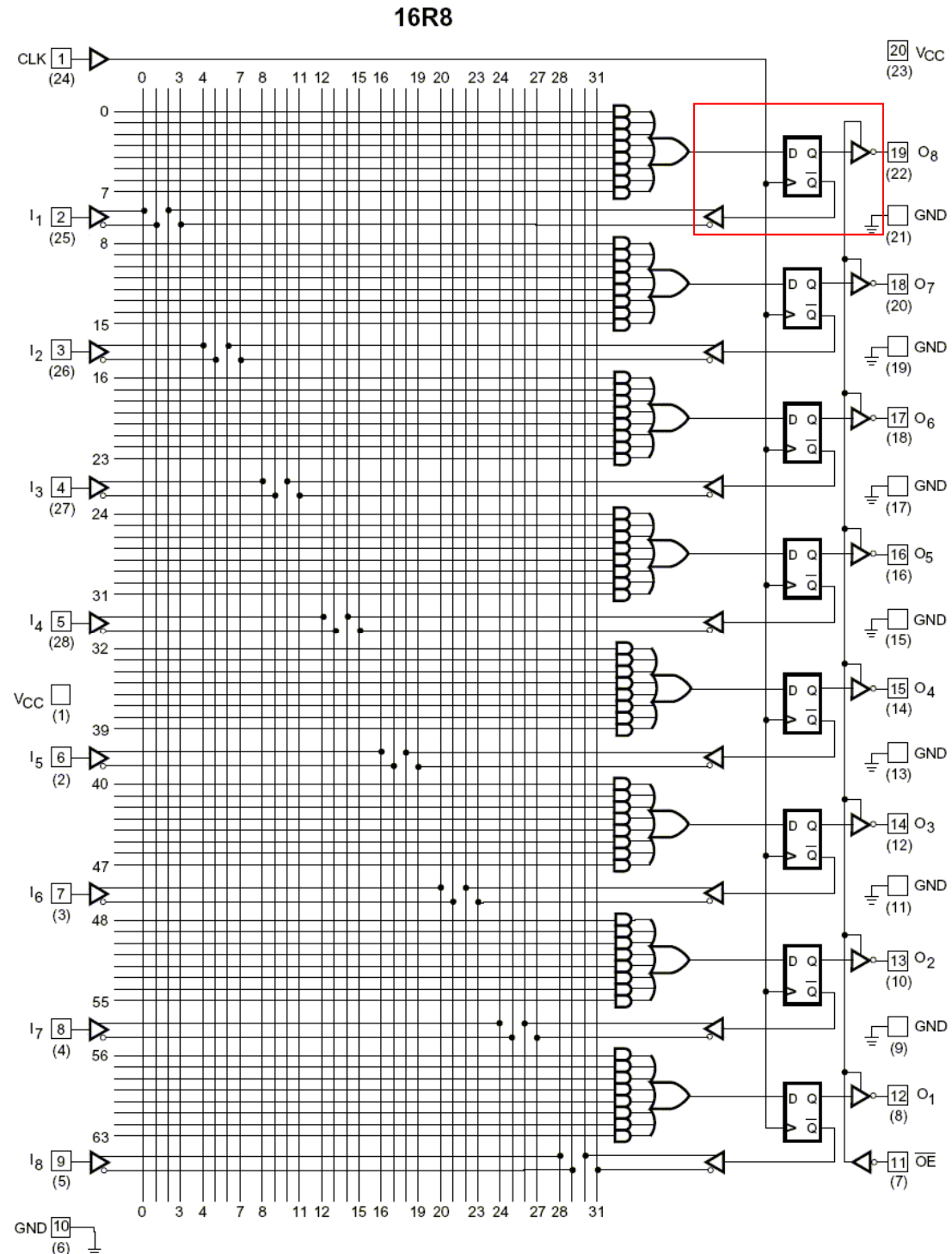- wire connection to a computer is needed
- once programmed, it will retain program
- does not need to be taken out of the circuit



## Complex Programmable Logic Devices *CPLD*

Complex *PLD*s (*CPLDs*) combine *PAL* combinational logic with FFs:


- organized as **logic blocks** connected via **programmable** connections
- **fixed OR** array size
- combinational or registered outputs
- enough logic for **simple counters**, **state machines**, **decoders**, etc
- while PAL/PLA are generally *One-time programmable* (**OTP**), many CPLDs are *electrically erasable* and *in-system reprogrammable* (**ISR**).
  - ISR CPLD devices placed in printed circuit boards (PCBs) can be fed it with a serial data stream from a personal computer.
  - ISR CPLD is able to decode the data stream and configure the CPLD to perform its specified logic function.
- Examples: 22G10, 20V8 (**check out the datasheets!**)

# GAL22V10 CPLD


**GAL:** Generic Array Logic

**Output Logic Macrocell (OLMC)** is user configurable

 - compatible with standard bipolar & CMOS devices
- **OLMC** / FF outputs can be **fed back**
- dedicated inputs
- *programmable* I/O lines






# GAL22V10 OLMC

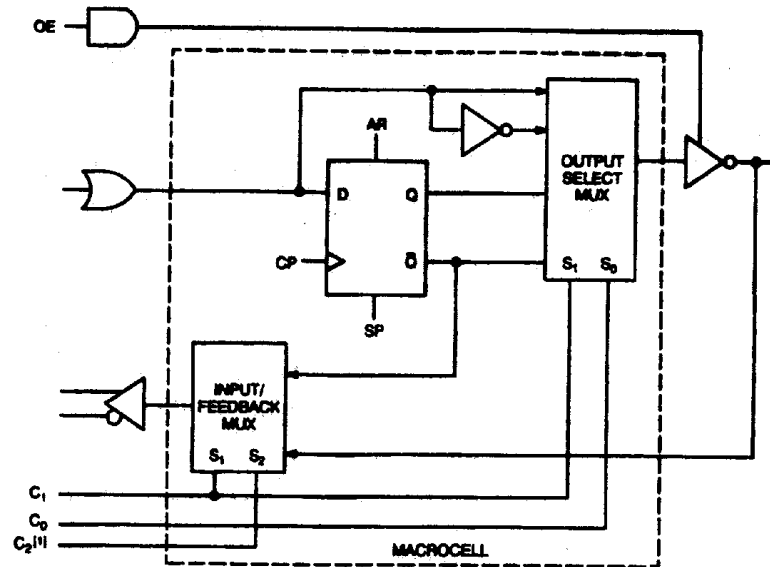


For each **OLMC** :

- variable product terms per **OLMC**
- product-term for output enable control
- output polarity can be **active high/ low**, in **combinatorial** or **registered** mode
- product term for **Asynchronous Reset (AR)** (sets registers to **zero** ) and for **Synchronous Preset (SP)** (sets registers to **one**) on **rising edge** of the next clock pulse.
- two modes: **registered** & **combinatorial I/O**
- **REGISTERED MODE**: **OLMC** output is driven by Q output of its D flip-flop
- **COMBINATORIAL I/O MODE**: **OLMC** output is driven by output of sum term gate. Feedback into the **AND** array is from the side of output enable buffer

   
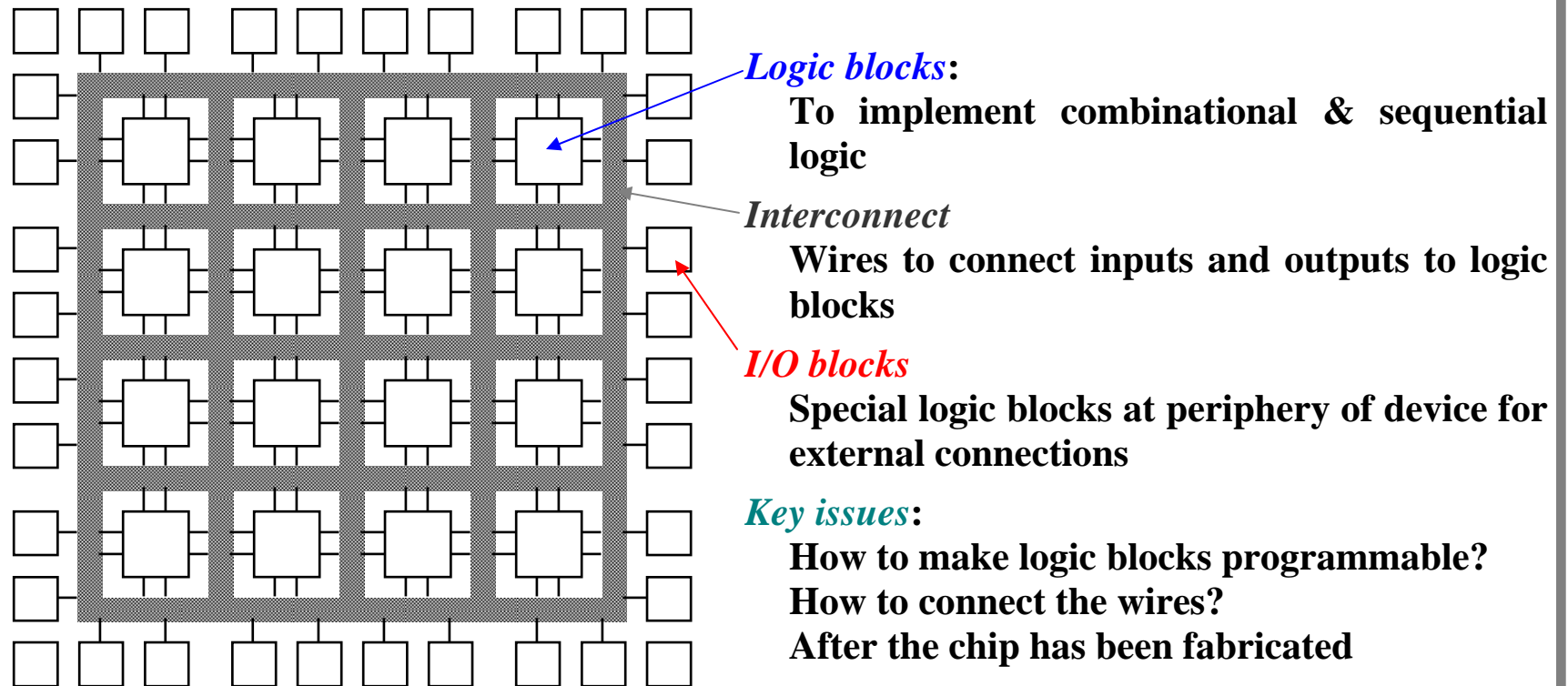
# Field Programmable Gate Array (FPGA)


**Field Programmable Gate Array FPGAs:** logic modules/blocks that are interconnected through **programmable connections**.



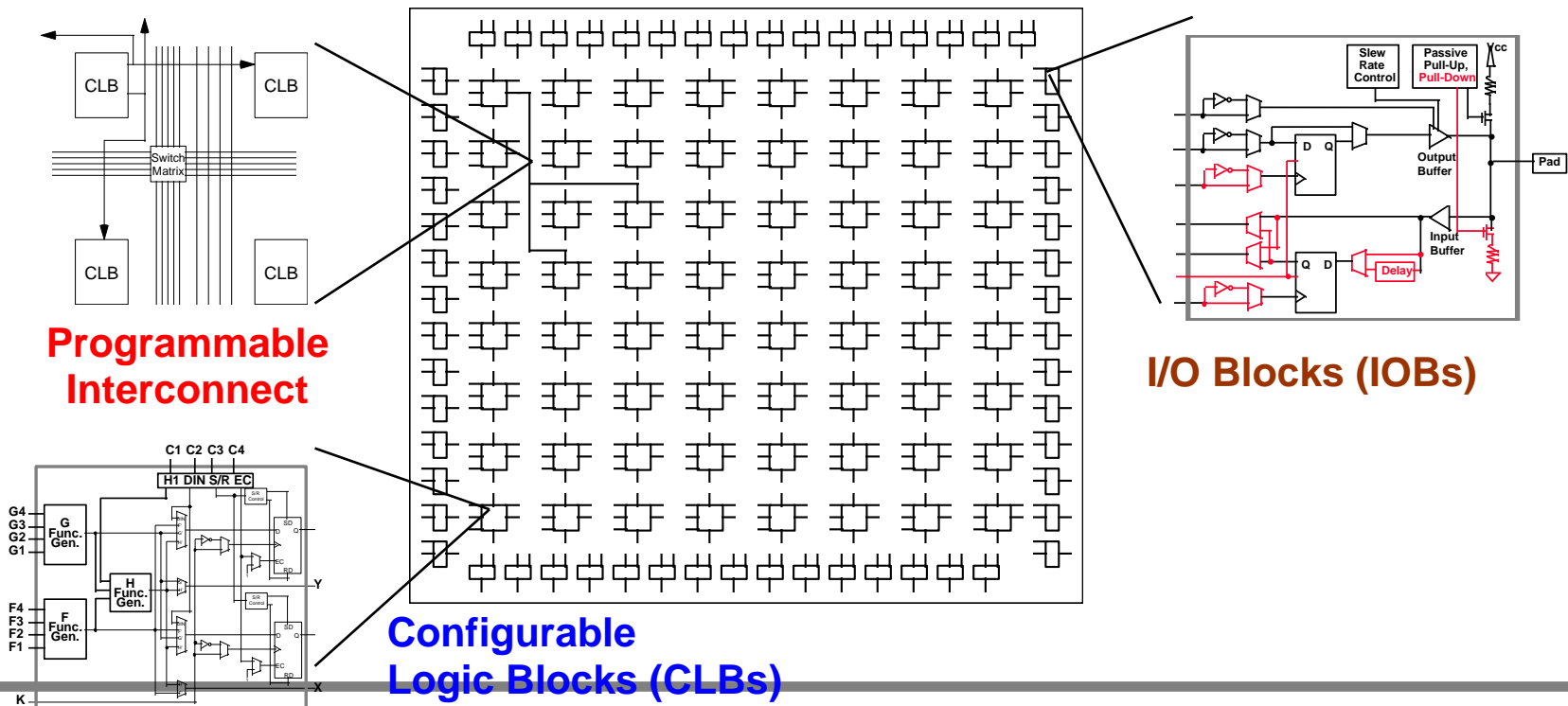
# Xilinx *FPGA*...

Xilinx *FPGAs* consist of **three** major segments

- **Configurable I/O Blocks (IOBs):** provide a programmable interface between internal logic array & I/O pins
- **Configurable Logic Blocks (CLBs):** perform user-specified logic functions
- **Interconnects:** programmed to form networks on the chip



# FPGA & CPLD Design Flow...

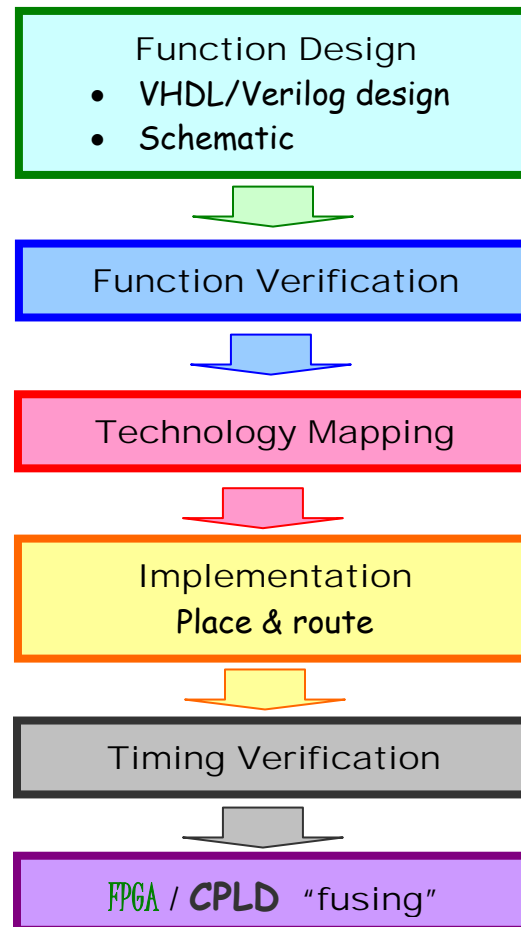

*system specification*

*For large volumes →  
Application Specific ICs  
(ASICs)*