 


## Tutorial PART 2 (SOLUTIONS)

NOTE THAT THERE ARE OTHER POSSIBLE SOLUTIONS TOO...

### SS1

Process only triggered/executed when there is an event on B (ie at T1,T2,T3). Note during the execution of process, signals do not change values while the variables can change. At T1,T2,T3: X changes based on "old value" of W while Z follows "new value" of Y. Also note the propagation delays for the output signals!



### SS2 (possible solutions)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- library call needed when using std logic functions
-- entity declaration

entity ss2 is
    port ( A,B,C,D : in  STD_LOGIC;
           X, Z : out STD_LOGIC);
end ss2;

architecture ss2arch of ss2 is
begin

    X <= A xor B xor C;

    Z <= (not (A) and B) or (not(B) and not(C) and D) or (not(B and D));

end ss2arch;
```

## Question 1

Behavioral modeling

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Z is 1 if A is a non-prime number
entity combcct is
    port( A : in std_logic_vector (3 downto 0); Z: out std_logic );
end combcct;

architecture beh of combcct is
begin
    process ( A )
    begin
        case (A) is
            when "0010" => Z <='0'; -- 2 is a prime number
            when "0011" => Z <='0';
            when "0101" => Z <='0';
            when "0111" => Z <='0';
            when "1011" => Z <='0';
            when "1101" => Z <='0';
            when others => Z <='1';
        end case;
    end process;
end beh;
-- any other solutions..?
```

## Question 2

```
entity customized_mux is
    port( A, B, C, D,E: in std_logic_vector(3 downto 0);
          S          : in std_logic_vector(2 downto 0);
          T          : out std_logic_vector(3 downto 0) );
end customized_mux;

architecture prog1 of customized_mux is -- architecture 1
begin
    -- in dataflow style of modeling
    with S select
        T <=  A    when "000",
              B    when "001",
              A    when "010",
              C    when "011",
              A    when "100",
              D    when "101",
              A    when "110",
              E    when others;
end prog1;

architecture prog2 of customized_mux is -- architecture 2
begin
    -- in behavioral style of modeling
    process ( S, A,B,C,D,E )
```

```

variable tmp: std_logic_vector(3 downto 0);
begin
  case S is
    when "000" => tmp:=A;
    when "001" => tmp:=B;
    when "010" => tmp:=A;
    when "011" => tmp:=C;
    when "100" => tmp:=A;
    when "101" => tmp:=D;
    when "110" => tmp:=A;
    when others => tmp:=E;
  end case;
  T <= tmp;
end process;
end prog2;

```

### Question 3

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity Dev_74138 is
  port (E1, E2, E3: in std_logic;
        A : in std_logic_vector (2 downto 0);
        Z : out std_logic_vector (0 to 7)); -- note that the order is Z(0), Z(1), Z(3).... Z(7).
end Dev_74138;
architecture BEH of Dev_74138 is
  begin
    process (A, E1, E2, E3) -- how would this work if A is not in the list? Would it still be a combinational cct?
      variable tmp : std_logic_vector (0 to 7);
      begin
        if E1 = '1' then Z <= "11111111";
        elsif E2 = '1' then Z <= "11111111";
        elsif E3 = '0' then Z <= "11111111";
        else
          case A is
            when "000" => tmp:= "01111111";
            when "001" => tmp:= "10111111";
            when "010" => tmp:= "11011111";
            when "011" => tmp:= "11101111";
            when "100" => tmp:= "11110111";
            when "101" => tmp:= "11111011";
            when "110" => tmp:= "11111101";
            when "111" => tmp:= "11111110";
            when others=> tmp:= "11111111";
          end case;
          Z <= tmp;
        end if;
      end process;
    end BEH;

```

#### Question 4

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity mul\_beh is

-- behavioral style of modeling

```
    Port ( x : in  STD_LOGIC_VECTOR (2 downto 0);
          y : in  STD_LOGIC_VECTOR (2 downto 0);
          z : out STD_LOGIC_VECTOR (5 downto 0));
end mul_beh;
```

architecture arch\_mul\_beh of mul\_beh is

begin

```
    process( x , y )
        variable w1,w2,w3, temp : std_logic_vector(5 downto 0);
    begin
```

```
        w1 := "000" & x(2) & x(1) & x(0);
```

```
        w2 := "00" & x(2) & x(1) & x(0) & '0';
```

```
        w3 := '0' & x(2) & x(1) & x(0) & "00";
```

```
        case y is
```

```
            when "000" => temp:= "000000";
```

```
            when "001" => temp:= w1;
```

```
            when "010" => temp:= w2;
```

```
            when "011" => temp:= w2+w1;
```

```
            when "100" => temp:= w3;
```

```
            when "101" => temp:= w3+w1;
```

```
            when "110" => temp:= w3+w2;
```


```
            when others => temp:= w3+w2+w1;
```

```
        end case;
```

```
        Z<=temp;
```

```
    end process;
```

```
end arch_mul_beh;
```

 

#### Question 5

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

entity Dev\_Encrpt is

```
port (D_in : in std_logic_vector (4 downto 0);   D_out : out std_logic_vector (2 downto 0) );
end Dev_Encrpt;
```

architecture BEH of Dev\_Encrpt is

begin

```
    process (D_in) -- work out another solution in dataflow style!!
```

```
    begin
```

```
        if D_in(3) = '0' and D_in(1) = '0' then D_out <= (D_in(4), D_in(2),D_in(0) );
```

```
        elsif D_in(3) = '0' and D_in(1) = '1' then D_out <= (D_in(0), D_in(4),D_in(2) );
```

```
        elsif D_in(3) = '1' and D_in(1) = '0' then D_out <= (D_in(2), D_in(0),D_in(4) );
```

```
        else D_out <= ( not(D_in(4)) , not(D_in(2)), not( D_in(0)) );
```

```
        end if;
```

```
    end process;
```

```
end BEH;
```

### SS3

**library** IEEE; -- VHDL program which realizes the circuit of Question 5 of Tutorial 5 (Part 1).  
**use** IEEE.STD\_LOGIC\_1164.ALL;

entity t5 is

Port ( B : in std\_logic\_vector ( 3 downto 0); N : out std\_logic\_vector (3 downto 0));  
end t5;

architecture Behavioral of t5 is

begin

process(B)

variable temp: std\_logic\_vector (3 downto 0);

begin

case B is

when "0000" => temp:="0011";  
when "0001" => temp:="0111";  
when "0010" => temp:="1000";  
when "0011" => temp:="0010";  
when "0100" => temp:="0110";  
when "0101" => temp:="1001";  
when "0110" => temp:="0000";  
when "0111" => temp:="1111";  
when "1000" => temp:="0101";  
when "1001" => temp:="0001";  
when "1010" => temp:="1010";  
when "1011" => temp:="0100";  
when "1100" => temp:="1011";  
when "1101" => temp:="1101";  
when "1110" => temp:="1100";  
when others => temp:="1110";


end case;

N <= temp;

end process;

end Behavioral;

### Question SS4


 


*Assumption:* The D input satisfies the set-up and hold times of the Latch and flip-flop. Also, the propagation delay of the devices are much less than the CLK period.



## Question 6

Connect D to J and  $\bar{D}$  to K.

## Question SS5

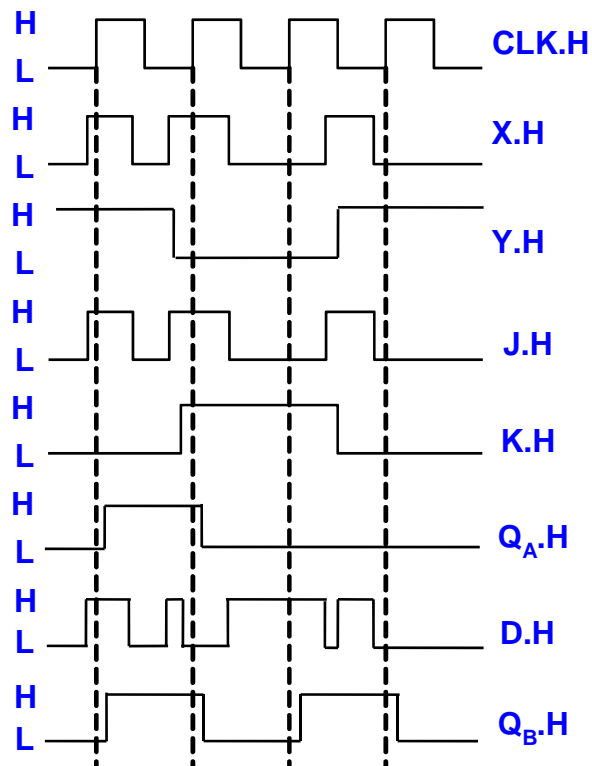 

### Question 7

  

A	B	Q	Q <sup>+</sup>
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Characteristic Table

A	B	Q <sup>+</sup>
0	0	1
0	1	Q
1	0	$\bar{Q}$
1	1	0

Condensed Characteristic Table

Q	Q <sup>+</sup>	A	B
0	0	X	1
0	1	X	0
1	0	1	X
1	1	0	X


Excitation Table

### Question 8

We need an extra JK flip-flop to implement a 5-bit counter. Such a counter would count from 0 to 31 and so to implement a mod29 counter, it needs to be cleared when count reaches 29:

$$29_{10} = (1 \ 1 \ 1 \ 0 \ 1)_2$$

 Since “11111” will not be reached for a mod-29 counter, the condition to be checked for is “111X1” i.e., we only need to detect  $Q_4 = Q_3 = Q_2 = Q_0 = 1$  to clear the counter. *How about for a Mod-27 counter?*



### Question 9 (next page)

### Question 10

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity count01_beh is
```

```
    Port (x, clk, rst : in std_logic;      y : out std_logic);
```

```
end count01_beh;
```

```
architecture count01_beh_arch of count01_beh is
```

```
begin
```

```
    process( clk , rst)
```

```
        -- assume that x synchronously changes with clock
```

```
        variable zeros_count: std_logic_vector (1 downto 0):= "00"; -- zeros_count
```

```
        variable ones_count: std_logic_vector (1 downto 0):= "00"; -- ones_count
```

```
    begin
```

```
        if (rst = '1') then y <= '0'; zeros_count := "00"; ones_count := "00";
```

```
        elsif (clk'event and clk = '1') then
```

```
            y <= '0'; --assigning a default value; else y will be 'U' until it becomes 1 or is reset.
```

```
            if (x = '0') and (zeros_count < "11") then zeros_count := zeros_count + '1';
```

```
            elsif (x = '1') and (ones_count < "11") then ones_count := ones_count + '1';
```

```
            end if;
```

```
            if (zeros_count = "11" and ones_count = "11") then y <= '1'; end if;
```

```
        end if;
```


```
    end process;
```

```
end count01_beh_arch;
```



## Question 9

4 mode 2-bit counter

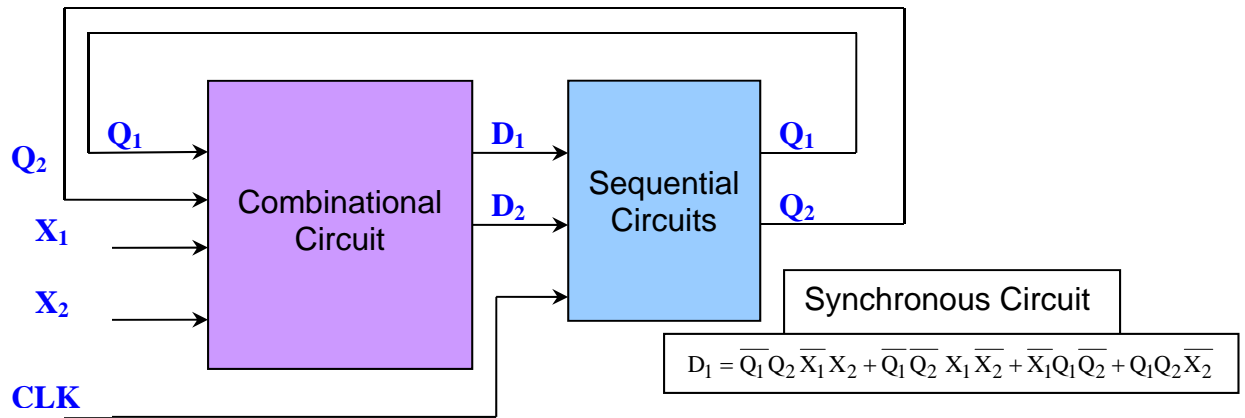


The next state table is:

$X_1$	$X_2$	$Q_1$	$Q_2$	$Q_1^+$ / $D_1$	$Q_2^+$ / $D_2$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0


$Q_1 Q_2$	00	01	11	10
$X_1 X_2$				
00	0	0	1	1
01	0	1	0	1
11	0	0	0	0
10	1	0	1	0

$Q_1 Q_2$	00	01	11	10
$X_1 X_2$				
00	0	1	1	0
01	1	0	0	1
11	0	0	0	0
10	1	0	0	1

 
$$D_2 = Q_2 \overline{X_1} \overline{X_2} + \overline{X_1} X_2 Q_2 + X_1 \overline{X_2} \overline{Q_2}$$



# Question 11

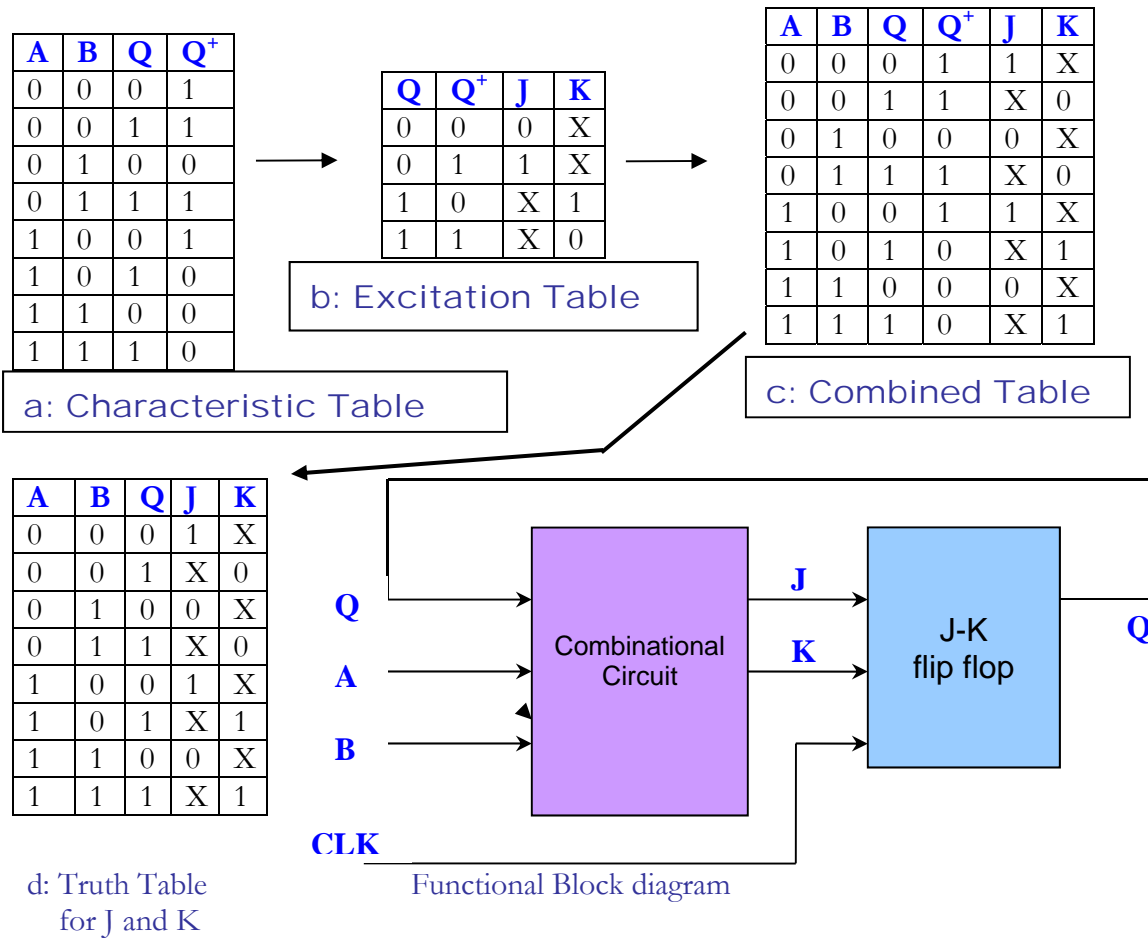

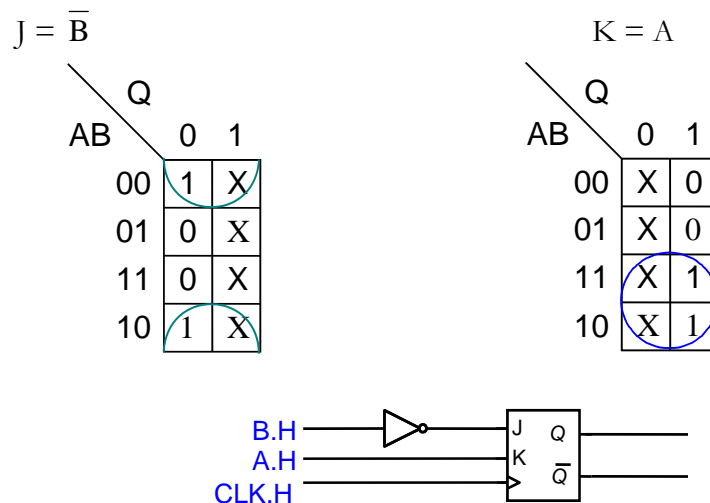e: Use Karnaugh Maps to find logic expressions of J and K



Attempt Question 6 following a similar procedure!

## Question 12

Previous value of X	Current value of X	Q+
0	0	Q
0	1	0
1	0	1
1	1	$\overline{Q}$

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity flipflop_beh is
  Port ( x : in std_logic;      clk : in std_logic;      y : buffer std_logic);
end flipflop_beh;

architecture flipflop_beh_arch of flipflop_beh is
begin

process( clk )
  variable xold, xnew, tmp: std_logic := '0';
begin
  if (clk'event and clk = '1') then
    xnew := x; tmp := y;
    if (xnew = '0' and xold = '1') then tmp := '1';
      elsif (xnew = '1' and xold = '0') then tmp := '0';
      elsif (xnew = '1' and xold = '1') then tmp := not tmp;
    end if;
    xold := xnew;
  y <= tmp;
  end if;
end process;
end flipflop_beh_arch;
```

## Question 13

A four-bit barrel shifter that can shift to the right by 0, 1, 2 or 3 positions.

1000  $\xrightarrow{\text{Shift right by 0 bit}}$  1000, 1000  $\xrightarrow{\text{Shift right by 1 bit}}$  0100  
1000  $\xrightarrow{\text{Shift right by 2 bit}}$  0010, 1000  $\xrightarrow{\text{Shift right by 3 bit}}$  0001

```
-- This particular barrel shifter is implemented as a combinational circuit
-- with a 4 bit input "data" and a 4 bit output "data_sft".
-- The "shift" input is a two bit vector that specifies whether
-- to shift the input by 0, 1, 2 or 3 positions to the right.

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity barrlshft_beh is
  Port ( data : in std_logic_vector(3 downto 0);
        shift : in std_logic_vector(1 downto 0);
        data_sft : out std_logic_vector(3 downto 0));
end barrlshft_beh;
```

```

architecture barrlshft_beh_arch of barrlshft_beh is
begin
process(data, shift)
begin
    case shift is
        when "00" => data_sft <= data;
        when "01" => data_sft <= '0' & data(3) & data(2) & data(1);
        when "10" => data_sft <= "00" & data(3) & data(2);
        when others => data_sft <= "000" & data(3);
    end case;
end process;
end barrlshft_beh_arch;

```


#### Question 14

The timing diagram of the pulse generator is as shown below. They are defined as follows:

Waveform 1: **Clock pulse**

Waveform 2: **Serial output for "1001 1001 0101 1110"**

 Waveform 3: **Synchronous load input (Indicates load operation)**



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity serial_sft is
    Port ( clk,rst,start_load : in std_logic;
          data : in std_logic_vector(15 downto 0); -- 16 bit input data
          shift_out : out std_logic); -- the bit being shifted out
end serial_sft;
--start_load loads the new data when asserted. Also wakes the system up from idle state
architecture serial_sft_arch of serial_sft is
    type states is (idle, serial_sft); --declaring the various states
    signal state: states;
    signal count: std_logic_vector(3 downto 0);

begin
    process (clk,rst)
        --asynchronous reset
        variable tmp: std_logic_vector(15 downto 0);
    begin
        if rst='1' then
            -- enter idle state if system is reset
            state <= idle; shift_out <= '0'; tmp := "0000000000000000"; count <= "0000";
        elsif clk'event and clk = '1' then
            case state is
                when idle =>
                    if start_load = '1' then -- parallel load the data & reset counter
                        state <= serial_sft; tmp:=data;
                        shift_out <= '0';count <= "0000";
                    end if;

                    when serial_sft =>
                        if start_load='1' then
                            tmp:=data; shift_out <= '0'; count <= "0000";
                        else shift_out <= tmp(conv_integer(count)); count := count+1;
                        end if; -- conv_integer is defined in library and required to
                        -- convert a vector to integer before it can be used as an index
                    end case;
            end if;
        end process;
    end serial_sft_arch;

```

## Question 15

The sequence is: ...0,2,6,7,5,0,2,6,7,5.... Thus, the next state table is as follows:

CURRENT STATE			NEXT STATE		
$Q2^N$	$Q1^N$	$Q0^N$	$Q2^{N+1}$	$Q1^{N+1}$	$Q0^{N+1}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	1	0	1
all other entries			X	X	X

However, as the PAL16R8 outputs are inverted,


$Q2^N$	$Q1^N$	$Q0^N$	$\overline{Q2^{N+1}}$	$\overline{Q1^{N+1}}$	$\overline{Q0^{N+1}}$
0	0	0	1	0	1
0	1	0	0	0	1
1	1	1	0	1	0
1	0	1	1	1	1
1	1	0	0	0	0
all other entries :			X	X	X

The D FF inputs are:

$$\begin{aligned} \text{D-FF \#2} &= \overline{Q1} \\ \text{D-FF \#1} &= \underline{Q0} \quad \underline{Q2} \\ \text{D-FF \#0} &= Q2 \quad Q0 + Q2 \quad \overline{Q1} \end{aligned}$$

Please note that only a rough simplification is done in the above solution, and the D-FF input expressions *can* be simplified further. However, we *need not* simplify if the resources (number of product terms etc) available on the PLD is sufficient to realize the circuit. OR-connections of the PAL are *not* programmable. To ensure that the output of the AND gates which are not in use remains de-asserted (low), we need the connections (★) as shown in the figure.

# 16R8

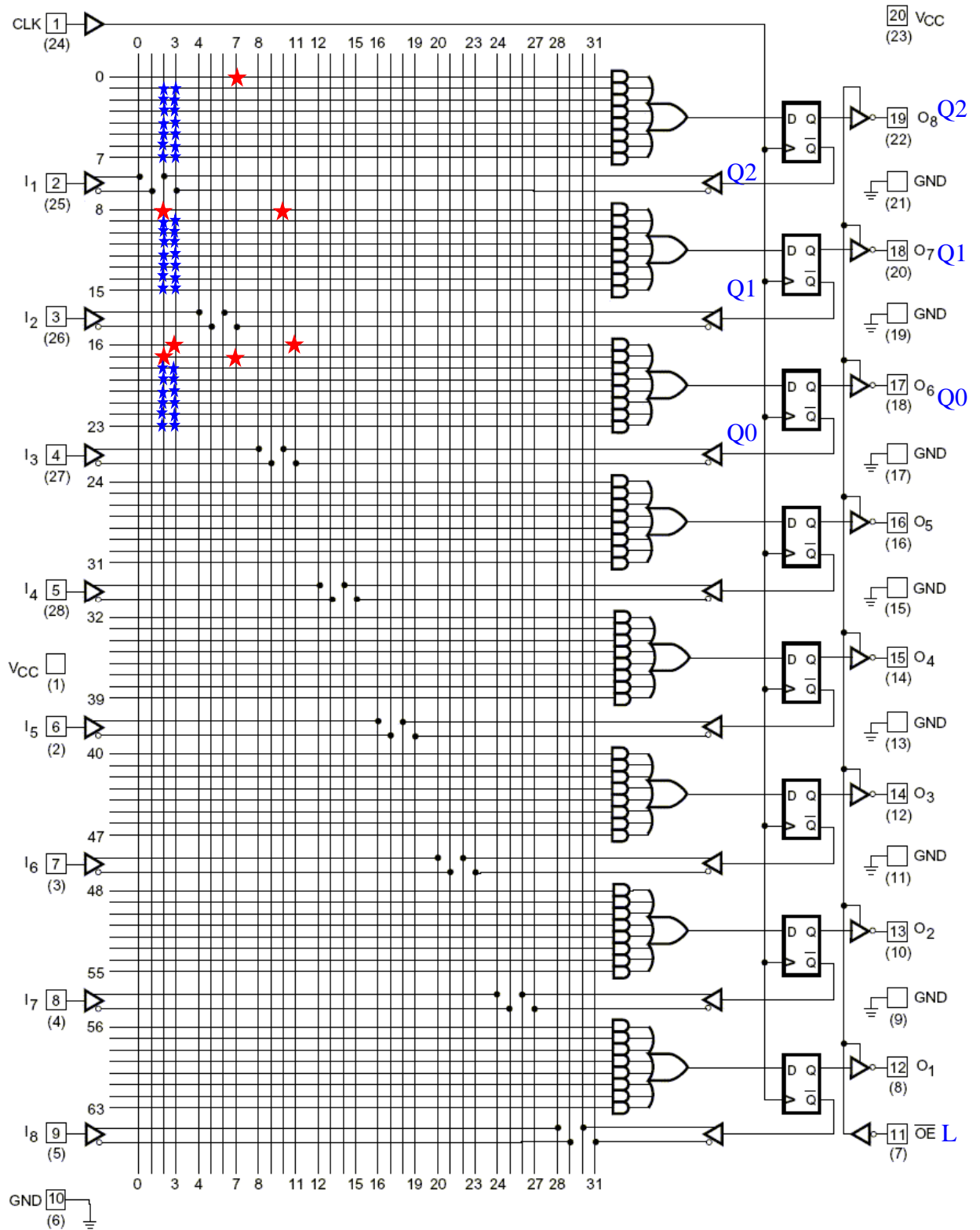


### Question 16

A	B	C	D	Z <sub>0</sub>	Z <sub>1</sub>	Z <sub>2</sub>
0	0	0	0	1	1	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	1	1	0
0	1	1	1	1	0	1
1	0	0	0	0	1	1
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	0	1	1	0	0	0
1	1	0	0	0	0	0
1	1	0	1	0	1	1
1	1	1	0	0	0	0
1	1	1	1	1	0	1

$$Z_0 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + ABCD$$

$$Z_1 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + AB\bar{C}\bar{D}$$
 
$$Z_2 = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + AB\bar{C}\bar{D} + ABCD$$



### Question 17

3K module needs to have 12 address lines  $A_{11}$ - $A_0$  and devices need to be enabled as follows:

$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$	$A_9$	$A_8$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$	
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	2K RAM
1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	Module
1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1K RAM
1	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	Module
1	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	Unused
1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	memory

{unshaded bits applied to address inputs of the RAM devices}

$$\begin{aligned}
 \text{Capacity of memory unit} &= \text{Number of memory locations} + \text{Number of bits per location} \\
 &= (2^{11} + 2^{10}) \times 8 \quad \{\text{i.e., } 3K \times 8 \text{ bits}\} \\
 &= 24\,576
 \end{aligned}$$


Memory range in use = Initial memory location  $\leftrightarrow$  Final memory Location  
 $= (8000H + 0000H) \leftrightarrow (8000H + 0BFFH)$   
 $= 8000H \leftrightarrow 8BFFH$

Unused memory range =  $(8000H + 0C00H) \leftrightarrow (8000H + 0FFFH)$   
 $= 8C00H \leftrightarrow 8FFFH$   
 (assuming that the memory map is till 8FFFH)

### Question 18

(a). ROM capacity =  $2^8 \times 8$

(b).

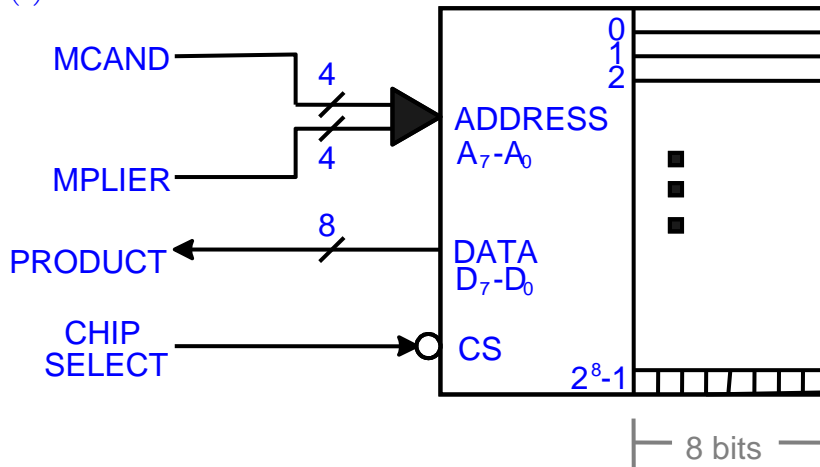

(c). The ROM contains  $2^8$  rows of 8 bit data. Each row is indexed by an address represented by MCAND and MPLIER and contains an 8 bit data of the corresponding PRODUCT.

### Question 19


A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1K RAM
1	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	Device1
1	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1K RAM
1	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	Device2
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1K RAM
1	0	0	0	0	1	0	1	1	1	1	1	1	1	1	1	Device3
1	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	1K RAM
1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	Device 4



From the above table, when A12 to A15 is “1000” the RAM module (i.e., one of the RAM devices) is enabled:

- the decoder is enabled
- A10 to A11 determines which decoder output (and thus RAM device) is active
- A0 to A9 applied to the address inputs of each RAM selects the particular location within the **selected** RAM device.

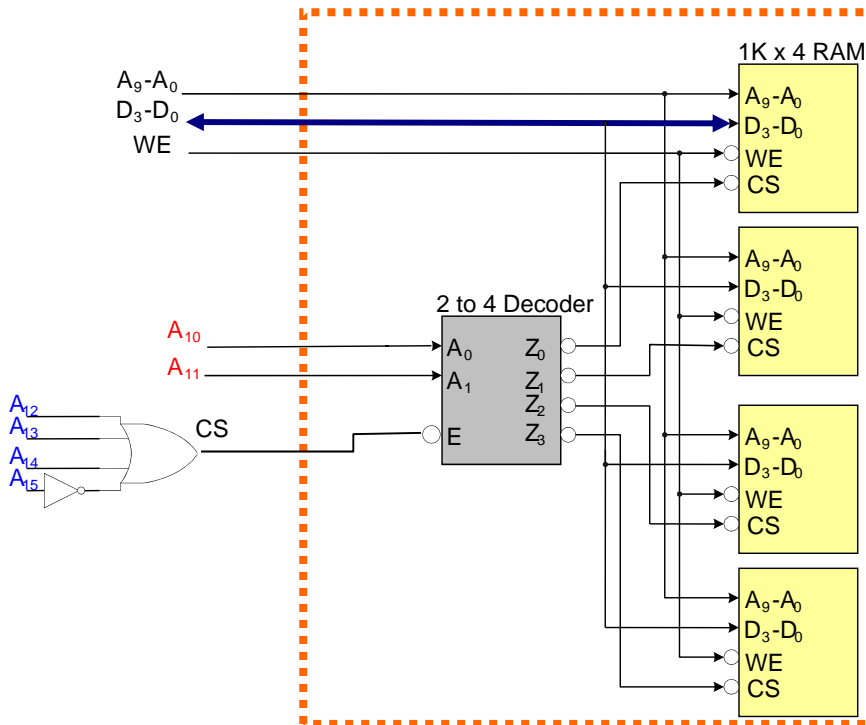4K x 4 RAM module (dotted box) with memory address starting from 8000H



*Is it possible to achieve exhaustive decoding by giving A<sub>1</sub>-A<sub>0</sub> as input to the 2-4 decoder instead of A<sub>11</sub>-A<sub>10</sub>?*