

# EE2020

## Digital Fundamentals

(L4: Gate-level Design & Minimization)

**Prof. Massimo Alioto**  
Dept of Electrical and Computer Engineering  
Email: *massimo.alioto@nus.edu.sg*

## Outline

- Gate-level logic design
- Karnaugh map
- Boolean function simplification using K-Map
- Gate-level implementation

# Gate-Level Logic Design

- Step 1 (simplify the Boolean function)
  - Simplify the Boolean function to be implemented
  - Methods of simplification
    - Postulates and theorem
    - Karnaugh Map
- Step 2
  - Implement the simplified Boolean function using logic gates
  - Minimize the gate counts
- Why minimization?
  - Cost, power, performance, size, reliability, ...


EE2020 Digital Fundamentals - XU YP

3
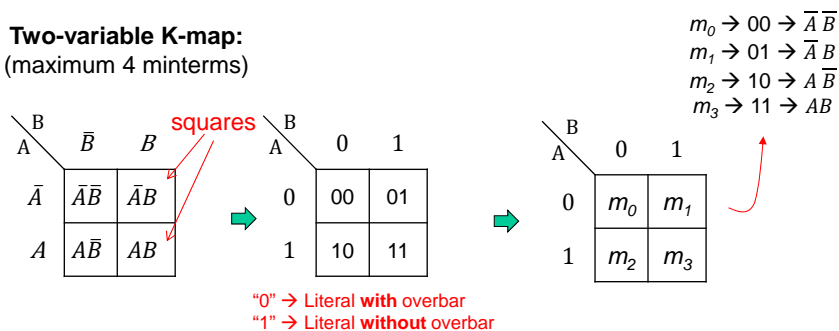
## Karnaugh Map (K-Map)

- K-map is a diagram that consists of a number of squares
- Each square represent one minterm (or maxterm) of a Boolean function
- The Boolean function (SOP) can be expressed as a sum of minterms in the map
- $n$ -variables Boolean function has maximum  $2^n$  minterms


**Two-variable K-map:**  
(maximum 4 minterms)



EE2020 Digital Fundamentals - XU YP

4

## Truth table → K-map

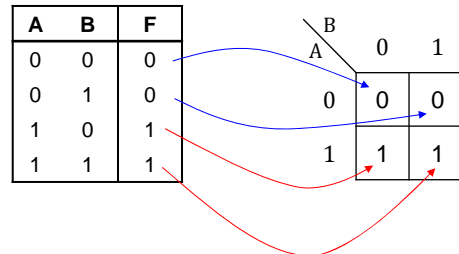

- K – map is a two-dimensional truth table
- Each row of in truth table corresponds to one square in the k-map
- If the term in a row is a *minterm* of the function ( $F=1$ ), place a “1” in the corresponding square of the K-map, otherwise (*maxterm*), place a “0”.

EE2020 Digital Fundamentals - XU YP

5

## Three- and four-Variable K-Maps

**\*Note that any two adjacent squares differ by only one literal**

**Three-variable K-map**

		BC			
		$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
A	$\bar{A}$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
	A	$A\bar{B}\bar{C}$	$A\bar{B}C$	$ABC$	$AB\bar{C}$

↓

		BC			
		00	01	11	10
A	0	000	001	011	010
	1	100	101	111	110

↓

		BC			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

**Four-variable K-map**

		CD			
		00	01	11	10
AB	00	0000	0001	0011	0010
	01	0100	0101	0111	0110
	11	1100	1101	1111	1110
	10	1000	1001	1011	1010

↓

		CD			
		00	01	11	10
AB	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

EE2020 Digital Fundamentals - XU YP

6

## Boolean function in K-map

Represent the following function on K-map:

$$F = \overline{A}B + AB + A\overline{B}$$

B \ A	0	1
0		
1		

Place a "1" in the square that represents a minterm in the given function

Write the Boolean expression for the function in K-map:

B \ A	0	1
0	0	1
1	1	0

$F = ?$

in SOP: write F as sum of the minterms (squares with "1")

## Boolean function in K-map (cont.)

Represent the following function on K-map:

$$F = \overline{A}BC + ABC + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$$

BC \ A	00	01	11	10
0	1	1	1	0
1	0	0	0	1

$$F = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$$

CD \ AB	00	01	11	10
00	1	0	1	1
01	0	1	0	0
11	1	0	0	0
10	0	1	1	1

Write the Boolean expression for the function in K-map:

BC \ A	00	01	11	10
0	1	0	0	0
1	0	1	0	0

$F = ?$

CD \ AB	00	01	11	10
00	0	1	0	0
01	0	0	0	1
11	0	1	0	0
10	0	0	0	0

$F = ?$

## Boolean function in K-map (cont.)

What about Boolean function in **non-canonical form**?

Example-1:

$$F = \overline{A}B + AB\overline{C} + \overline{A}BC$$

$$\overline{A}B = \overline{A}B(C + \overline{C}) = \overline{A}BC + \overline{A}B\overline{C}$$

BC \ A	00	01	11	10
0				
1				

Or  $\overline{A}B \rightarrow 01, C = 0 \text{ or } 1$

or just fill the truth table and derive the K-map

Example-2:

$$F = A + \overline{A}\overline{B}CD + B\overline{C}\overline{D}$$

CD \ AB	00	01	11	10
00				
01				
11				
10				


EE2020 Digital Fundamentals - XU YP

9
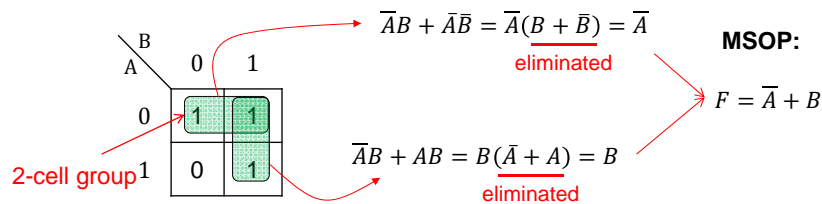
## Boolean function simplification using K-map

Boolean function (SOP) simplification using K-map

Simplify:  $F = \overline{A}B + AB + \overline{A}\overline{B}$



Alternatively,

$$\begin{aligned} F &= \overline{A}B + AB + \overline{A}\overline{B} \\ &= \overline{A} + AB \\ &= \overline{A} + B \end{aligned}$$

\*The variable that changes value in the group is eliminated, or the variable that doesn't change value in the group remains

EE2020 Digital Fundamentals - XU YP

10

## Boolean function (SOP) simplification using K-Map (cont.)

Three-variables:

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + ABC$$



$$F = \bar{A} + B\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} &\rightarrow \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B(C + \bar{C}) \\ &\rightarrow \bar{A}\bar{B} + \bar{A}B \rightarrow \bar{A}(\bar{B} + B) \rightarrow \bar{A} \end{aligned}$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} \rightarrow (\bar{A} + A)\bar{B}\bar{C} \rightarrow \bar{B}\bar{C}$$



$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + ABC$$



$$F = \bar{B} + \bar{A}\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} &\rightarrow \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B(\bar{C} + C) \\ &\rightarrow (\bar{A} + A)\bar{B} \rightarrow \bar{B} \end{aligned}$$
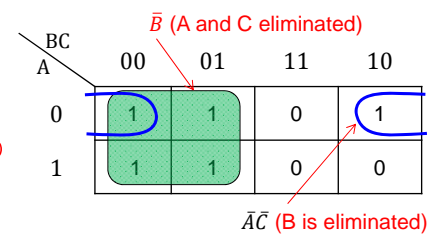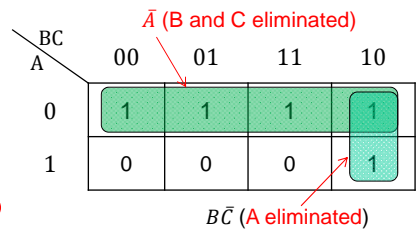
$$\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} \rightarrow \bar{A}(\bar{B} + B)\bar{C} \rightarrow \bar{A}\bar{C}$$



EE2020 Digital Fundamentals - XU YP

Group the adjacent cells where only one variable changes value so that it can be eliminated

11

## Minimization (SOP) using K-Map (cont.)

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}B\bar{C}D + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}CD$$





$$F = \bar{B}\bar{C}\bar{D} + BD + CD$$

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}B\bar{C}D + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}CD$$



$$F = \bar{B}\bar{D} + BD$$

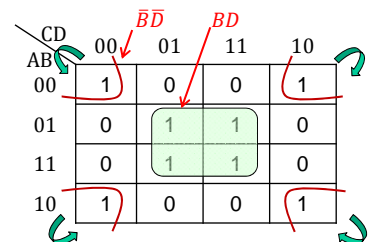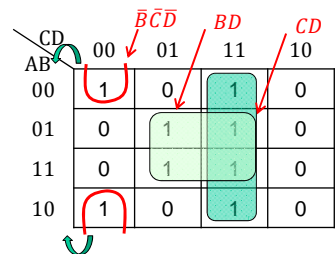

EE2020 Digital Fundamentals - XU YP

12

# Minimization (SOP) using K-Map (cont.)

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ + \bar{A}BCD + \bar{A}BC\bar{D} + \bar{A}B\bar{C}D + \bar{A}BCD \\ + ABCD + ABC\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D}$$

$$F = B + \bar{D}$$

CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

Grouping rules:

- Group the squares that only contains "1"
- Groups must be either horizontal or vertical (diagonal is invalid)
- Group size is always  $2^n$ , that is, 2, 4, 8, ...
- Group should be as large as possible (contains as many as squares with "1" as possible)
- Each square with "1" must be part of a group if possible
- Simplified term retains those variables that don't change value
- Variables that change value in the group are eliminated

EE2020 Digital Fundamentals - XU YP

13

## Invalid groupings

CD \ AB	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

Squares in the group are not in power of two

Two variable change value

CD \ AB	00	01	11	10
00	0	1	0	1
01	1	0	0	1
11	0	1	1	1
10	0	1	1	1

It's not horizontal or vertical

EE2020 Digital Fundamentals - XU YP

14

## Don't-care condition

- So far we assume that all combination of the input variables of a Boolean function are valid (for example, 3-variable Boolean function has 8 different input combinations that makes the function equal to 0 or 1)
- There are applications in which some variable combinations never appear.
- One of such examples is the BCD code
  - 4-bit BCD code can have 16 values
  - However, 1010 – 1111 are never used, or  $\bar{A}\bar{B}C\bar{D}$ ,  $\bar{A}\bar{B}CD$ ,  $A\bar{B}C\bar{D}$ ,  $A\bar{B}CD$ ,  $AB\bar{C}\bar{D}$ , and  $AB\bar{C}D$  never occur
- These conditions are called **don't-care conditions**.
- Don't-care condition is marked with "X" in K-map
- For minimization, X can take either "1" or "0".

Binary-Coded Decimal (BCD)

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

## Minimization with don't-care conditions

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}CD$$



$$F = B + \bar{D}$$

CD \ AB	00	01	11	10
00	1	0	0	1
01	X	1	X	1
11	X	1	X	1
10	1	0	0	1

Assume X = 1

\*Treat X = 1 and group the squares as usual



## Minimization (POS) using K-Map (cont.)

### Boolean function in POS:

$$F = (A + B + C + \bar{D})(A + B + \bar{C} + D) \\ (A + \bar{B} + C + D)(A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D) \\ (\bar{A} + B + C + \bar{D})(\bar{A} + B + \bar{C} + D)$$

$$F = (\bar{C} + D)(B + C + \bar{D})(\bar{B} + C + D)$$

maxterm: complement (0=NOT(x))

CD \ AB	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

$$(A + B + C + \bar{D}) \cdot (\bar{A} + B + C + \bar{D}) \\ = A\bar{A} + \bar{A}(B + C + \bar{D}) \\ + A(B + C + \bar{D}) = (B + C + \bar{D})$$

### POS simplification using K-map:

- Group the squares that only contains "0"
- Form an OR term (sum) for each group, instead of a product
- Value "1", instead of "0", represent complement of the variable,
- Follow similar grouping rules for SOP
- Either SOP or POS can be used to implement the Boolean function, depending on which gives more efficient implementation.

summarizing: proceed as SOP, but group 0's instead of 1's (square = maxterm)  
+ complement the values in row-col. to find maxterm associated with square

EE2020 Digital Fundamentals - XU YP

17

## Minimal SOP (MSOP)

### Some terminologies

Implicant, prime implicant and essential implicant

#### • Implicant of a Boolean function

- Each product term in SOP is called an implicant of the function

Example-1:

$$F(a,b,c) = ab + \bar{a}bc + a\bar{b}c + \bar{c} + abc$$

Implicants

Literals

Example-2:

BC \ A	00	01	11	10
0	1	1	0	0
1	1	1	1	0

How many implicants?

EE2020 Digital Fundamentals - XU YP

18

## Minimal SOP (MSOP) – Prime implicant

- **Prime implicant**

- An implicant that cannot be combined with another term to eliminate a variable

Example-1:

$$F = AB + ABC + BC$$

Non-prime implicant (already contained in AB or BC)  
 Prime implicants

Example-2:

	CD	00	01	11	10
AB	00	0	1	1	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$\bar{A}\bar{B}D$ ,  $\bar{A}BD$  and  $\bar{A}B\bar{D}$

are implicants, but not prime implicants  
(can be grouped into larger groups of 4)

$\bar{A}D$  and  $\bar{A}\bar{B}$  are essential prime implicants

graphically: prime implicant grouping  
cannot be expanded further (but could  
overlap with other prime implicants)

EE2020 Digital Fundamentals - XU YP

19

## Identifying prime implicants

- A single “1” on a K-map is a prime implicant if it is not adjacent to any other 1 of the function.
- Two adjacent “1”s represent a prime implicant, provided that they are not within a rectangle of 4 or more squares containing “1”s.
- Four “1”s that are an implicant are a prime implicant if they are not within a group of 8 squares containing “1”s

Basically, implicant is prime if it cannot be enclosed  
within a larger square/rectangle (as per K-map rules)


EE2020 Digital Fundamentals - XU YP

20
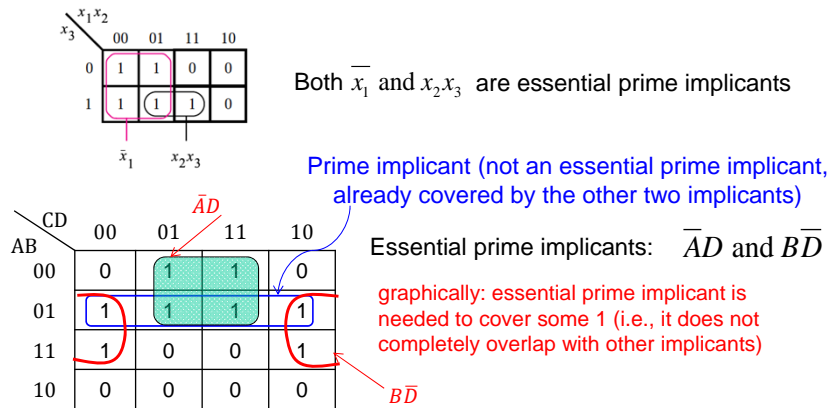
## Essential prime implicant

- **Essential prime implicant**

- A prime implicant that is not included in any other prime implicant



EE2020 Digital Fundamentals - XU YP

21

## Minimal SOP Expression (MSOP)

- What is MSOP?
  - It contains a minimal number of literals and terms
  - All essential prime implicants must be included in MSOP
- Determination of MSOP
  - Finding all of the *prime implicants* of the function
  - Select essential prime implicants (those with “1”s that have only been grouped once)
  - Finding a minimal subset of these prime implicants that covers all of the *minterms* of the function

EE2020 Digital Fundamentals - XU YP

22

## Obtaining MSOP - examples

### Example – 1:

CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

Essential Prime implicant



Select the essential prime implicant with minimum set of prime implicants

All implicants including **one** essential prime implicant

CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

## Obtaining MSOP - examples (cont.)

### Example – 2:

CD \ AB	00	01	11	10
00	0	0	1	0
01	1	0	1	1
11	1	1	1	1
10	0	0	1	0

Essential Prime implicant



Select the essential prime implicant with minimum set of prime implicants

All implicants including **two** essential prime implicant

CD \ AB	00	01	11	10
00	0	0	1	0
01	1	0	1	1
11	1	1	1	1
10	0	0	1	0

## Obtaining MSOP - examples (cont.)

### Example – 3:

CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	0	1	0
10	1	0	1	1

Essential  
Prime implicant

Essential  
Prime implicant

All implicants including  
**two** essential prime implicant



Select the essential prime implicant  
with minimum set of prime implicants

CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	0	1	0
10	1	0	1	1

## Gate-level implementation


- NAND only implementation
- NOR only implementation

## NAND only implementation


Logic operation:



NAND implementation:


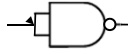


$$\overline{x \cdot x} = \overline{x}$$

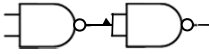

$$F = A\overline{B} + \overline{C}D$$

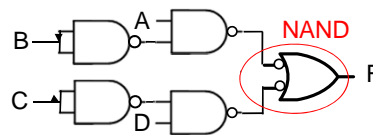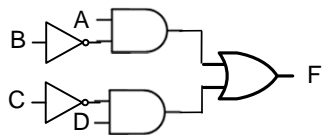- Replace the OR gate with NAND gate and balance the bubble
- Replace the inverter with NAND gate




EE2020 Digital Fundamentals - XU YP



27
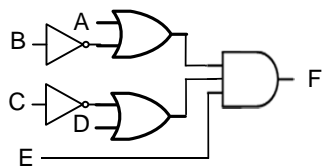
## NAND only implementation – cont.


$$F = (A + \overline{B}) \cdot (\overline{C} + D) \cdot E$$



Add double bubble → Do nothing

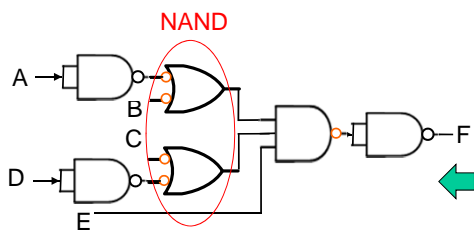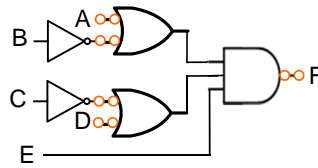

Replace inverters with NAND gates

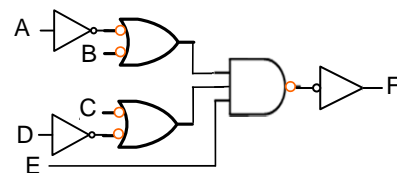

EE2020 Digital Fundamentals - XU YP


28

## NOR only implementation


Logic operation:



NOR implementation:


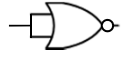


$$\overline{x + x} = \overline{x}$$

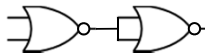

$$F = (A + \overline{B}) \cdot (\overline{C} + D) \cdot E$$

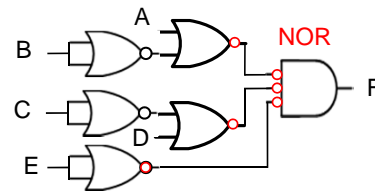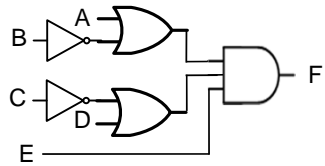- Replace the AND gate with NOR gate and balance the bubble
- Replace the inverter with NOR gate






EE2020 Digital Fundamentals - XU YP

29


## NOR only implementation – cont.

$$F = A\overline{B} + \overline{C}D$$

Add double bubble → Do nothing

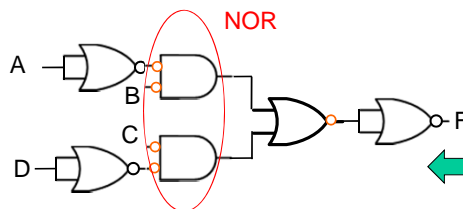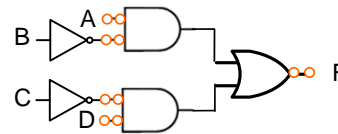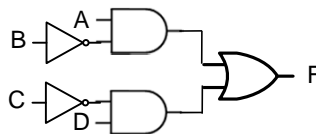

Replace inverters with NOR gates

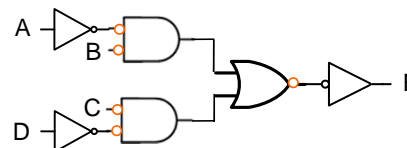


EE2020 Digital Fundamentals - XU YP

30
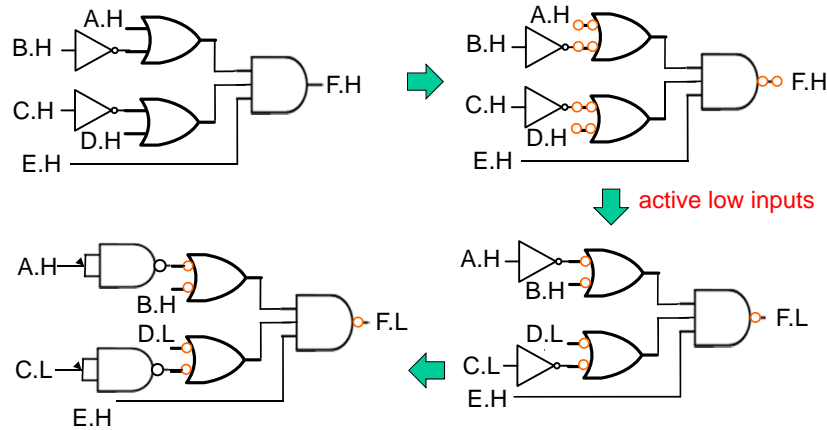
## NAND only Implementation with Mixed Logic

$$F = (A + \bar{B}) \cdot (\bar{C} + D) \cdot E \quad (\text{where C, D and F are active low})$$




EE2020 Digital Fundamentals - XU YP

31
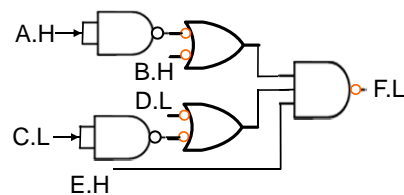
## NAND only implementation with Mixed Logic – cont.

Write the Boolean function implemented by the circuit below and express F in positive logic.



EE2020 Digital Fundamentals - XU YP

32



# Summary

- Karnaugh map
- Boolean function simplification using K-map
  - SOP simplification
  - POS simplification
  - Don't-care condition
  - Minimal SOP (MSOP) and POS (MPOS)
- Gate-level implementation
  - NAND only
  - NOR only