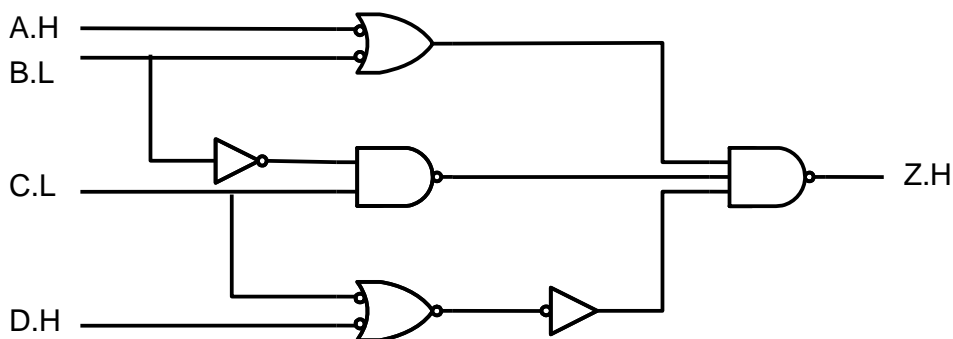


Tutorial 3 - Questions (Part 1)


Logic gates

1. Use algebraic manipulation to find the MSOP for $f = x_1x_3 + x_1\bar{x}_2 + \bar{x}_1x_2x_3 + \bar{x}_1\bar{x}_2\bar{x}_3$.
2. For circuits 1 and 2 below:
 - (a) Fill in all the intermediate signal names using the positive logic convention
 - (b) Find the logic expression for Z for the two cases.

Circuit 1



Circuit 2

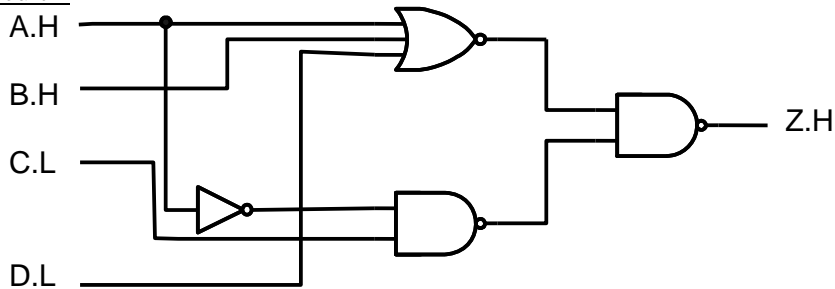

3. Design a logic circuit using only NOR gates. Use alternate gate representation if necessary for clear circuit diagrams.

$$X = A \oplus B \oplus C$$
4. Design a circuit to realize $Z = \bar{A}B + \bar{B}\bar{C}D + \bar{B}\bar{D}$ in the positive logic convention. A and B are active low signals while C, D and Z are active high. Use a minimum number of gates, and draw clear circuit diagrams with alternate gate representations as required.