 


Tutorial PART 2 (SOLUTIONS)

NOTE THAT THERE ARE OTHER POSSIBLE SOLUTIONS TOO...

20. i) Design based on J-K FF



Next state table (from the problem specification):


X(t)	x(t-1)	Q	Q+
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

We need to use the excitation table of the J-K FF


Q	Q ⁺	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

The truth table for the combination circuit is:

X(t)	x(t-1)	Q	Q+	J	K
0	0	0	1	1	x
0	0	1	0	x	1
0	1	0	1	1	x
0	1	1	1	x	0
1	0	0	0	0	x
1	0	1	0	x	1
1	1	0	0	0	x
1	1	1	1	x	0

 

 Now, how to get X_{t-1} from X_t ? Use D-FF.





ii) Design based on D-FF

The next state table $X_{t-1}, X_t, Q \rightarrow Q+$ remains same as before.


With D FF, the truth table for the combination circuit is:

$X(t)$	$x(t-1)$	Q	$Q+ / D$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

  

D-FF design needs more components than J-K FF design because D-FF is capable of only very simple behavior compared to J-K, i.e. $D=Q+$ vs. hold, set, reset and toggle.

21.

 

	IN	
	0	1
S ₀	S ₁	S ₂
S ₁	S ₂	S ₂
S ₃	S ₀	S ₀
S ₂	S ₀	S ₀

		IN	
		0	1
C ₁ C ₀	00	1	0
	01	0	0
	11	0	0
	10	0	0

		IN	
		0	1
C ₁ C ₀	00	0	1
	01	1	1
	11	0	0
	10	0	0


	C ₁	C ₀
S ₀	0	0
S ₁	0	1
S ₂	1	0
S ₃	1	1

Next State Table for
Min Risk Design

State Assignment

$$C_0^+ = \overline{C_1} \overline{C_0} \overline{IN} \quad C_1^+ = \overline{C_1} IN + \overline{C_1} C_0$$
 
$$OUT1 = S_0 IN + S_1 = \overline{C_1} \overline{C_0} IN + \overline{C_1} C_0 \quad OUT2 = S_2 = C_1 \overline{C_0}$$



VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ASMPROB2 is
    Port ( INP : in  STD_LOGIC; --in is a reserved word
          CLOCK: in  STD_LOGIC; OUT1: out STD_LOGIC; OUT2: out STD_LOGIC);
```

```

end ASMPROB2;


architecture Arch_ASMPROB2 of ASMPROB2 is
type states is (S0, S1, S2);
signal state:states;
begin

process(clock)
begin
if clock'event and clock = '1' then
    case state is
        when S0=>
            OUT2 <= '0';
            if INP = '0' then
                state <= S1;
                OUT1 <= '0';
            else
                state <= S2;
                OUT1 <= '1';
            end if;
        when S1 =>
            state <= S2;
            OUT1 <= '1';
        when S2 =>
            state <= S0;
            OUT1 <= '0';
            OUT2 <= '1';
        end case;
    end if;
end process;
end Arch_ASMPROB2;


```

SS10

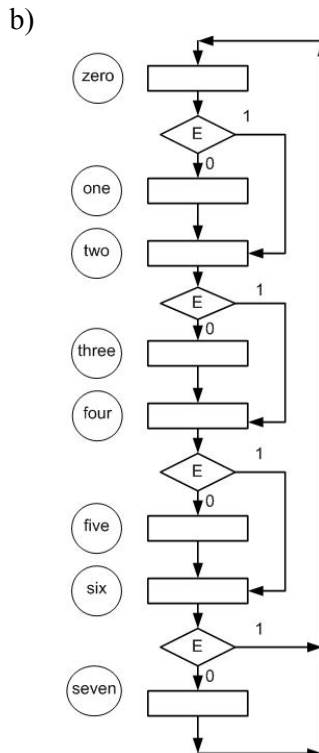(a) **Synchronous input** → the input signal changes value only “at” the active clock edge, i.e the clock is one of the signals that is causing the input to change value. In practice, the input will not change value exactly at the clock edge, but after a small propagation delay t_{pd} (few nanoseconds).




 (c) In state 2, if $E=0$ the next state will be state 3. The value of $E=0$ in the clock cycle corresponding to state 2, just before the next clock edge comes will make the machine goto state 3. The machine will go to state 3 t_{pd} after the next edge. (See figure below)



d)


E	Q2	Q1	Q0	Q2+ / D0	Q1+ / D1	Q0+ / D0
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	1
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	1	1	0
0	1	1	0	0	1	1
0	1	1	1	0	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	0	0	0
1	1	1	1	0	0	0

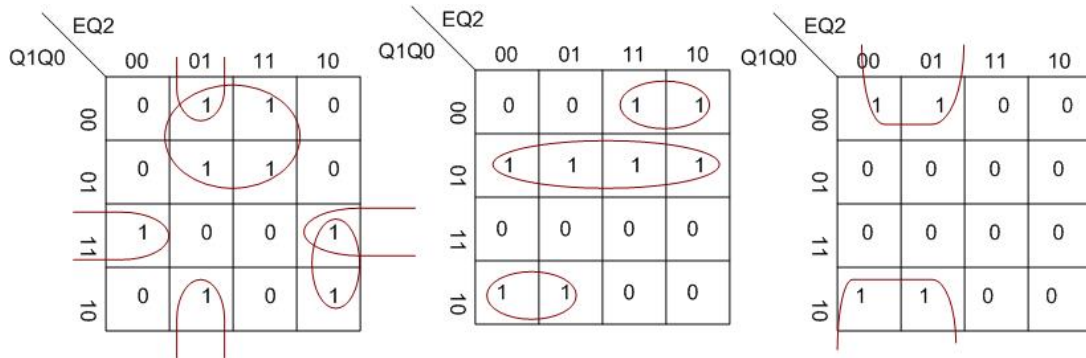


$$D_2 = Q_2 \bar{Q}_1 + E \bar{Q}_2 Q_1 + \bar{Q}_2 Q_1 Q_0 + \bar{E} Q_2 Q_0$$

$$D_1 = \bar{Q}_1 Q_0 + E \bar{Q}_1 + \bar{E} Q_1 Q_0$$

$$D_0 = \bar{E} \bar{Q}_0$$

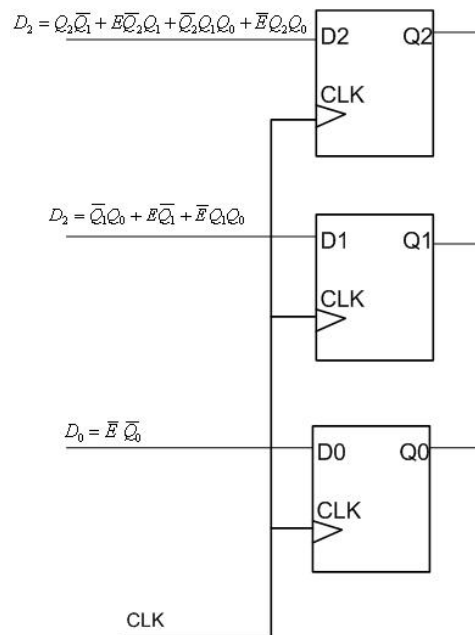


e)

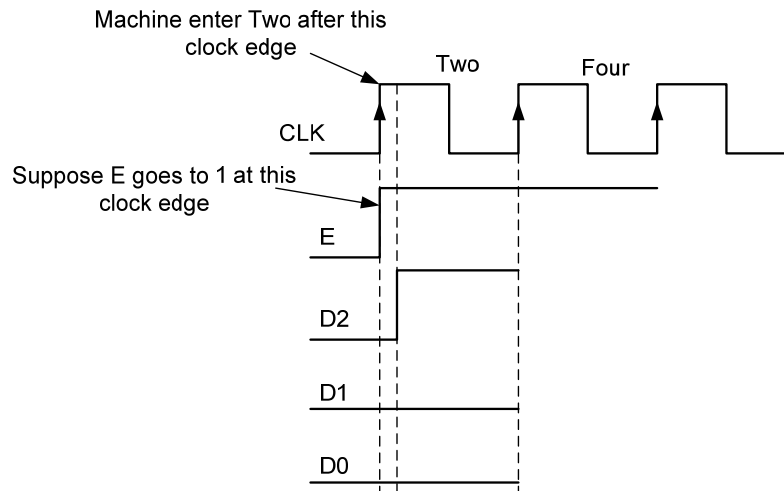


For $E=1$, $Q_2=0$, $Q_1=1$ and $Q_0=0$, the combinational circuit will calculate $D_2=1$, $D_1=0$, $D_0=0$ after t_{pd} (as shown).

These signals are waiting at the respective FF inputs. When the next clock edge comes, the machine will goto $Q_2^+=1$, $Q_1^+=0$ and $Q_0^+=0$, i.e. state Four.

 f) $TC = \overline{E}Q_2Q_1Q_0 + EQ_2Q_1\overline{Q_0}$



22.

 

	I ₁ , I ₂			
	00	01	11	10
SA	SB	SB	SC	SC
SB	SA	SD	SB	SB
SC	SA	SA	SA	SA
SD	SB	SB	SB	SB

Next State
Table

	C ₁	C ₀	State Assignment
SA	0	0	
SB	0	1	
SC	1	0	
SD	1	1	

Traditional Method

Excitation Equations

		I ₁ I ₂			
		00	01	11	10
C ₁ C ₀	00	1	1	0	0
	01	0	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$C_0^+ = \bar{I}_1 \bar{C}_1 \bar{C}_0 + C_1 C_0 + C_0 I_2 + I_1 C_0$$

		I ₁ I ₂			
		00	01	11	10
C ₁ C ₀	00	0	0	1	1
	01	0	1	0	0
	11	0	0	0	0
	10	0	0	0	0


$$C_1^+ = \bar{C}_1 \bar{C}_0 I_1 + \bar{C}_1 C_0 \bar{I}_1 I_2$$

Output Equations

From ASM chart:

$$\begin{aligned}
 OUT1 &= SA + SB.I_1 \\
 &= \bar{C}_1 \bar{C}_0 + \bar{C}_1 C_0 I_1 \\
 &= \bar{C}_1 \bar{C}_0 + \bar{C}_1 I_1
 \end{aligned}$$

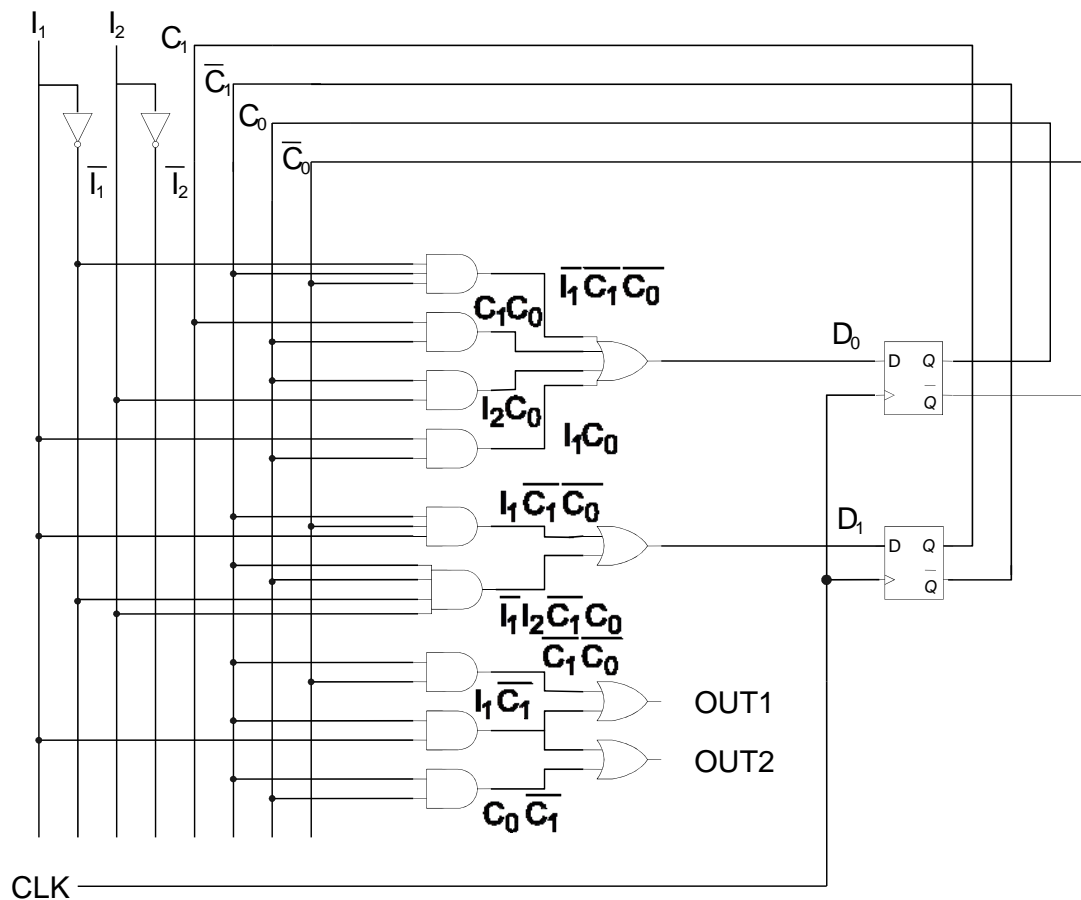
$$\begin{aligned}
 OUT2 &= SA.I_1 + SB \\
 &= \bar{C}_1 \bar{C}_0 I_1 + \bar{C}_1 C_0 \\
 &= \bar{C}_1 C_0 + \bar{C}_1 I_1
 \end{aligned}$$



PLA Based Design

Given the 4-input, 4-output, 8 AND-term PLA, we can realize the combinational circuit required for the state generator with it, and realize the output logic separately. Or we can challenge ourselves to see if all of the combinational logic for the state generator as well as the output can be realized entirely with the PLA. If you count all the AND terms that will be required to implement the latter, you will find that you need 12 AND gates; however, the PLA has only 8 AND gates.

 Below, it is shown, how we can group minterms selectively with Karnaugh maps to reduce the total number of AND terms required to less than 8. The strategy is to have as many common groupings as possible from the 4 maps.




		$I_1 I_2$			
		00	01	11	10
$C_1 C_0$	00	1	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	0	0


$$OUT1 = \overline{C_1} \overline{C_0} \overline{I_1} + \overline{C_1} \overline{C_0} I_1 + \overline{C_1} C_0 I_1$$

$C_1 C_0$		$I_1 I_2$			
		00	01	11	10
00	0	0	1	1	
01	1	1	1	1	
11	0	0	0	0	
10	0	0	0	0	

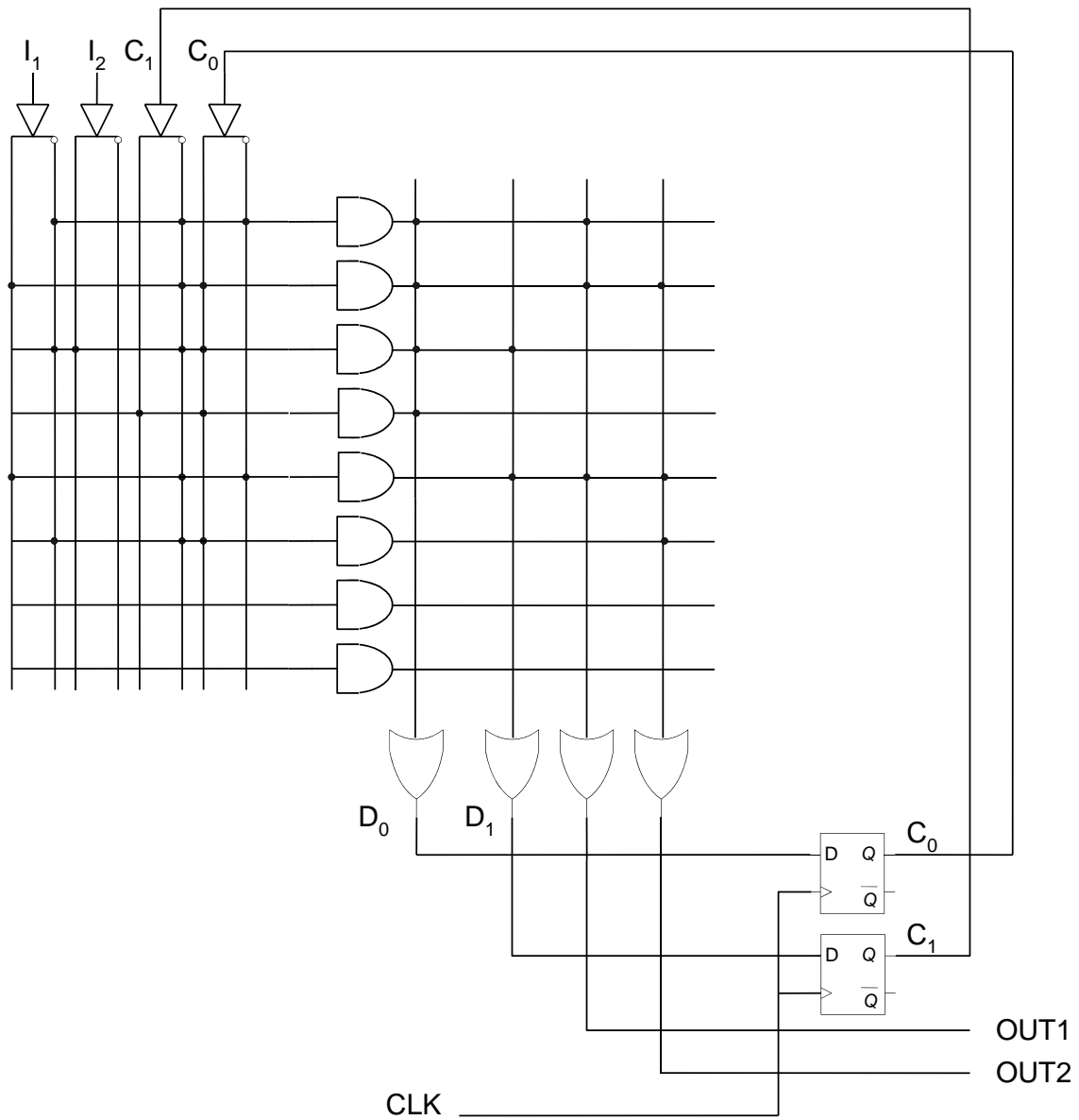
$$OUT2 = \overline{C_1} C_0 \overline{I_1} + \overline{C_1} \overline{C_0} I_1 + \overline{C_1} C_0 I_1$$



23.

 

(a). State MC block diagram

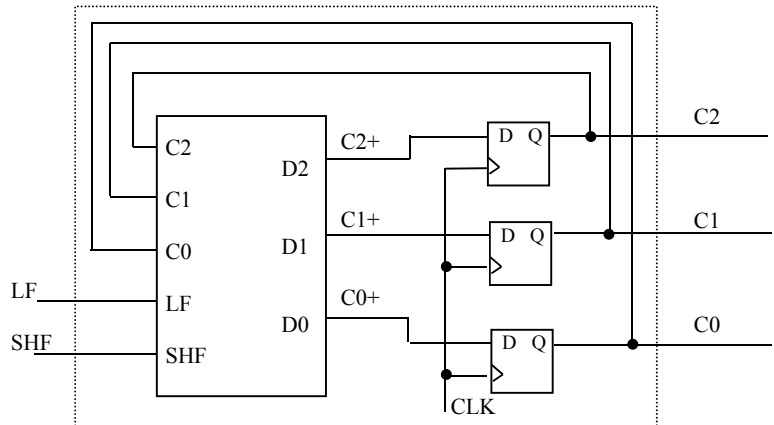

(b). State generator block diagram

(c). Make the following state assignments (arbitrary)

S0: 000, S1: 001, S2: 010, S3: 011, S4: 100

Then construct the next state table based on assigned states.


The idea is to use a ROM to realize the combinational circuit of the state generator as well as the output signals. Specifically, we will use the current state bits ($C_2C_1C_0$) and the inputs (LF and SHF) as the address signals of a ROM. Each memory location will have 7 bits of data, viz. C_2+ , C_1+ , C_0+ (the next state bits) and REG.LD, ALU.C1, Z1 and Z0 (4 output signal bits). This will require us to use a ROM with 32×7 capacity. Construct the next state table as follows (by inspection of the ASM chart).

C2	C1	C0	LF	SHF	C2+ (D2)	C1+ (D1)	C0+ (D0)	REG.LD	ALU.C1	Z1	Z0
0	0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	1	0	1	0	1	0	0	1
0	0	0	1	X	0	1	1	1	0	0	0
0	0	1	X	X	0	1	0	0	1	0	0
0	1	0	X	X	0	0	0	0	0	0	0
0	1	1	X	0	1	0	0	0	1	0	0
0	1	1	X	1	0	1	1	0	1	1	0
1	0	0	X	X	0	0	0	0	0	0	0

Now make the following correspondence between ROM address inputs and data outputs
Also decide that if controller ever gets into states 5,6 or 7 a transition to state S0 is made.

ROM Addr. Input	Signal Name
A4	C2
A3	C1
A2	C0
A1	LF
A0	SHF


Data Output	Signal Name
D6	C2+ (D2)
D5	C1+ (D1)
D4	C0+ (D0)
D3	REG.LD
D2	ALU.C1
D1	Z1
D0	Z0

 


24.

For the architectural elements, we choose 2 counters: (a) A decade counter with synchronous clear and terminal count output. (b) A mod-300 counter with synchronous clear and a terminal count output.

Architectural components

 


$TC_1 \rightarrow 1$ on count of 9

 

$TC_2 \rightarrow 1$ on count of 299

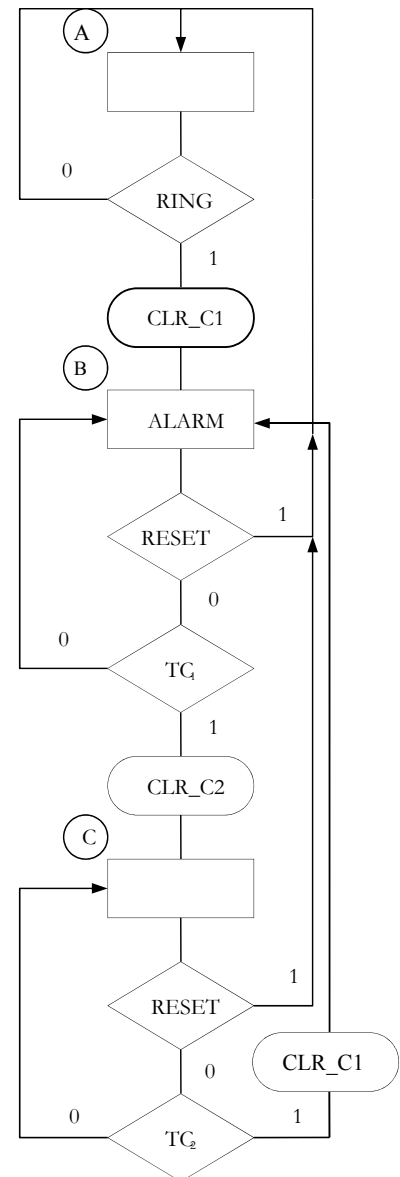ASM Chart for hardware realization using architectural components.



VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- this is a VHDL realization of the Alarm Clock state machine
-- ASM Chart for this realization can be easily inferred

entity ALARM_CLOCK is
    Port ( RING : in  STD_LOGIC;
          CLOCK : in  STD_LOGIC;
          RESET : in  STD_LOGIC;
          ALARM : out STD_LOGIC);
end ALARM_CLOCK;


architecture Arch_ALARM_CLOCK of ALARM_CLOCK is
    type states is (IDLE, RING_ALARM, WAITING);
    --WAIT is a VHDL reserved word and shouldn't be used as a state name
    signal state:states;
begin

    process(clock) --synch state machine
        variable counter1 : std_logic_vector(3 downto 0); -- 10 seconds
        variable counter2 : std_logic_vector(8 downto 0); -- 300 seconds
    begin
        if clock'event and clock = '1' then
            case state is
                when IDLE =>
                    ALARM <= '0';
                    if RING = '1' then
                        state <= RING_ALARM;
                        counter1 := "0000";
                    end if;
                when RING_ALARM =>
                    ALARM <= '1';
                    if RESET = '1' then
                        state <= IDLE;
                    elsif counter1 = 9 then
                        state <= WAITING;
                        counter2 := (others=>'0');
                        --easier way to write counter2 <= "000000000";
                    else
                        counter1 := counter1+1;
                    end if;
                when WAITING =>
                    ALARM <= '0';
                    if RESET = '1' then
                        state <= IDLE;
                    elsif counter2 = 299 then
                        state <= RING_ALARM;
                        counter1 := "0000";
                    else
                        counter2 := counter2+1;
                    end if;
            end case;
        end if;
    end process;
end Arch_ALARM_CLOCK;
```

SS11 Write a *VADL* program which realizes the circuit and verify its performance using available simulation tools.

25.

ASM Chart

 

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity PEOPLE_COUNTER is
port(CLOCK, RESET, ENTER, LEAVE :in std_logic;
      FULL, EMPTY: out std_logic);
end PEOPLE_COUNTER;

architecture Arch_PEOPLE_COUNTER of PEOPLE_COUNTER is
type states is (state0, statel, state2, state3);
signal state: states;
begin
process (CLOCK, RESET)
variable enterleave: std_logic_vector(1 downto 0) := "00";
begin
if RESET='1' then
    state <= state0; -- asynchronous reset
    FULL <= '0'; EMPTY <= '1';
elsif (CLOCK'event and CLOCK='1') then
enterleave(0):=LEAVE;
enterleave(1):=ENTER;
    case state is
        when state0 => -- zero person in room .. initial state
            if ENTER = '1' then
                state <= statel;
                FULL <= '0'; EMPTY <= '0';
            end if;
        when statel => -- one person in room
            case enterleave is
                when "00" => state <= statel;
                when "10" => state <= state2;
                when "01" => state <= state0; EMPTY <= '1';
                when others => state <= statel;
            end case;
        when state2 => -- two persons in room
            case enterleave is
                when "00" => state <= state2;
                when "10" => state <= state3; FULL <= '1';
                when "01" => state <= statel;
                when others => state <= state2;
            end case;
        when state3 => -- three persons in room
            if LEAVE = '1' then
                state <= state2;
                FULL <= '0';
            end if;
        end case;
    end if;
end process;
end Arch_PEOPLE_COUNTER;
-- Note: in ASM charts, output signals appear in states where they are to be asserted ("conditional" or "unconditional")
--       however, in the VHDL programs, these output signals remain at '1' or '0' until they are updated.
```